

# Analog Filters


© Jiří Hospodka

Czech Technical University in Prague



KATEDRA TEORIE OBVODŮ  
Fakulta elektrotechnická


# Old Electronic circuits

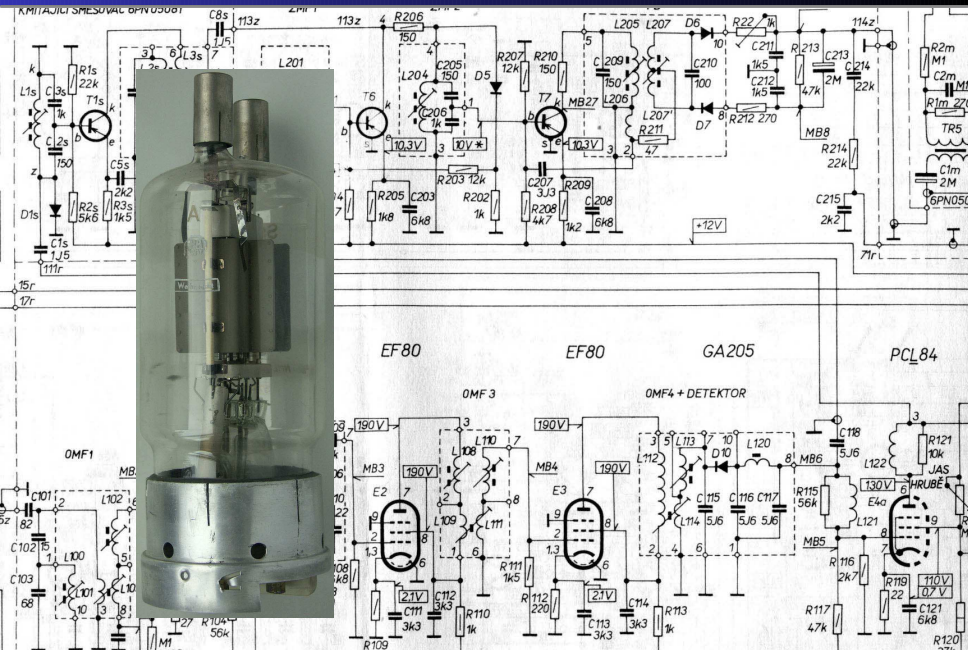

## Where the analog filters are used?

- Anti-aliasing filters – before sampling (and conversion to digital) of analog signal,
- In communication – frequency multiplex  $\equiv$  transmitting multiple signals (with different frequency) over a single line – for special applications or high frequency signals, where digital filters cannot be used,
- Interference (DC component, 50 Hz, noise, ...) suppression,
- Reconstruction filters, conversion of digital signals back to analog signal.


# Sampling of analog signals

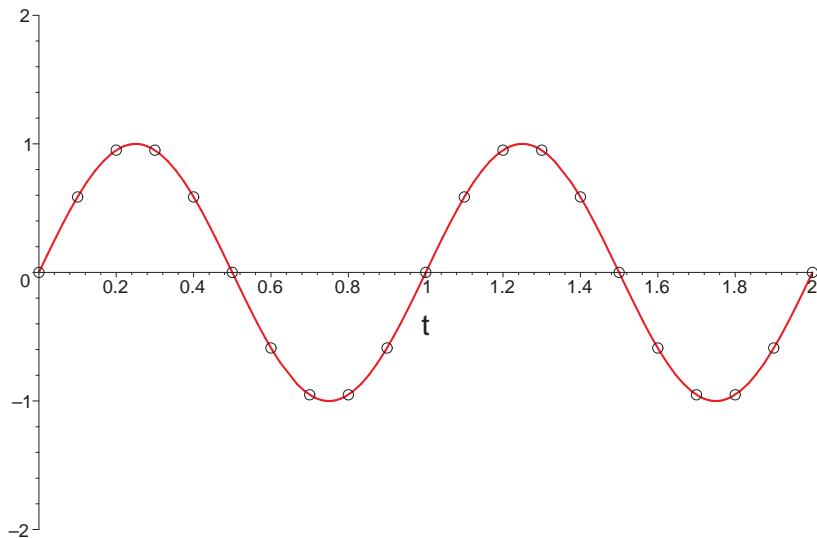

$f_c = 10$ , resp.  $f_c/2 = 5$

$\sin(2\pi 1t)$


## Sampling of analog signals

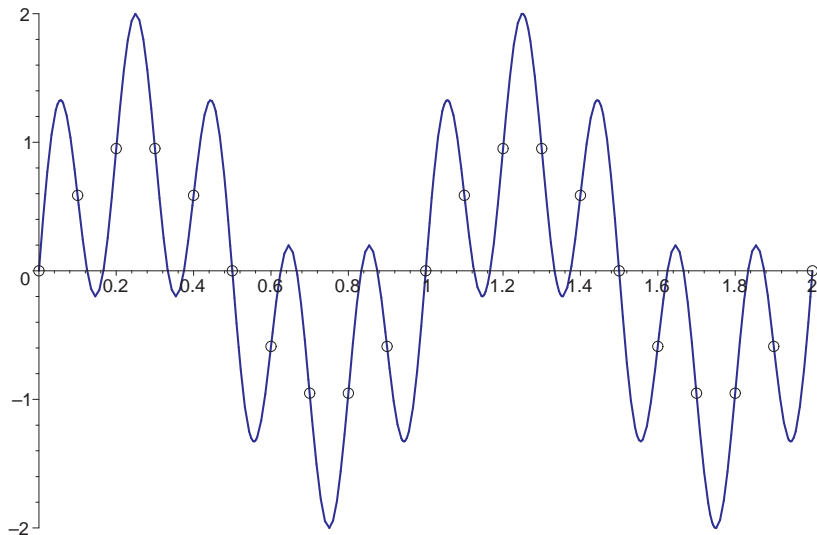

$f_c = 10$ , resp.  $f_c/2 = 5$


$$\sin(2\pi 1t) + \sin(2\pi 5t)$$

## Sampling of analog signals

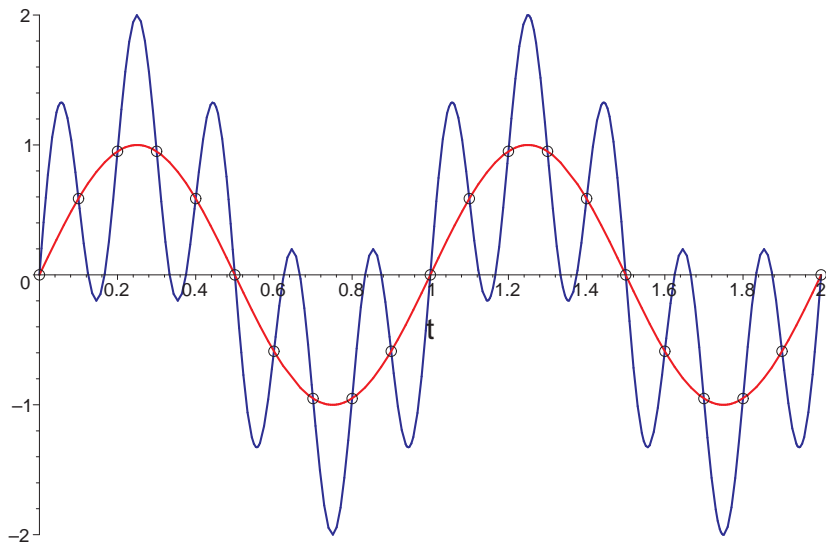

$f_c = 10$ , resp.  $f_c/2 = 5$   $\sin(2\pi 1t) + \sin(2\pi 5t)$ , resp.  $\sin(2\pi 1t)$


# Sampling of analog signals

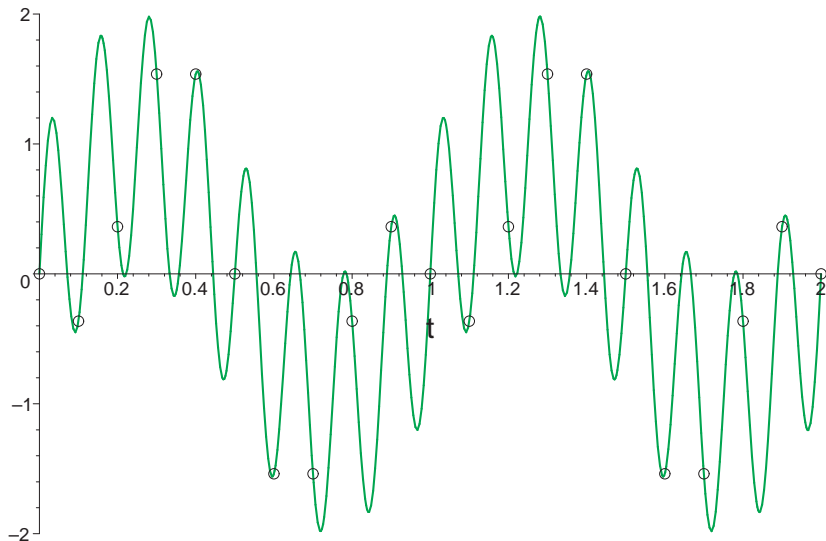

$f_c = 10$ , resp.  $f_c/2 = 5$

$$\sin(2\pi 1t) + \sin(2\pi 8t)$$

# Sampling of analog signals

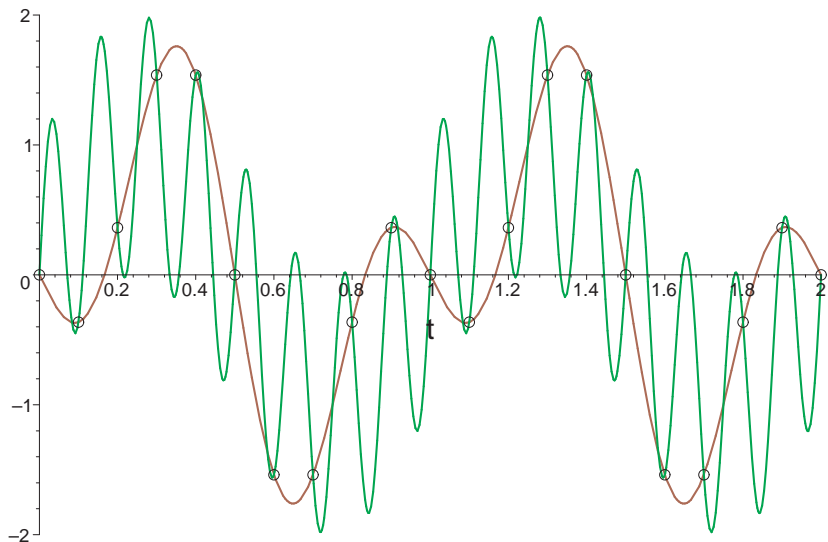


$$f_c/2 = 5$$


$$\sin(2\pi t) + \sin(2\pi 8t), \text{ resp. } \sin(2\pi 1t) - \sin(2\pi 2t)$$



# Sampling of analog signals

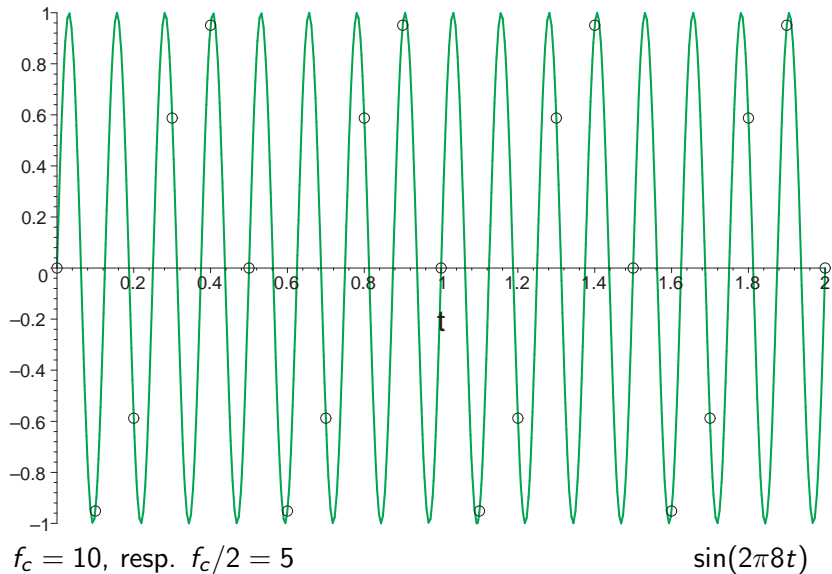


## Sampling of analog signals

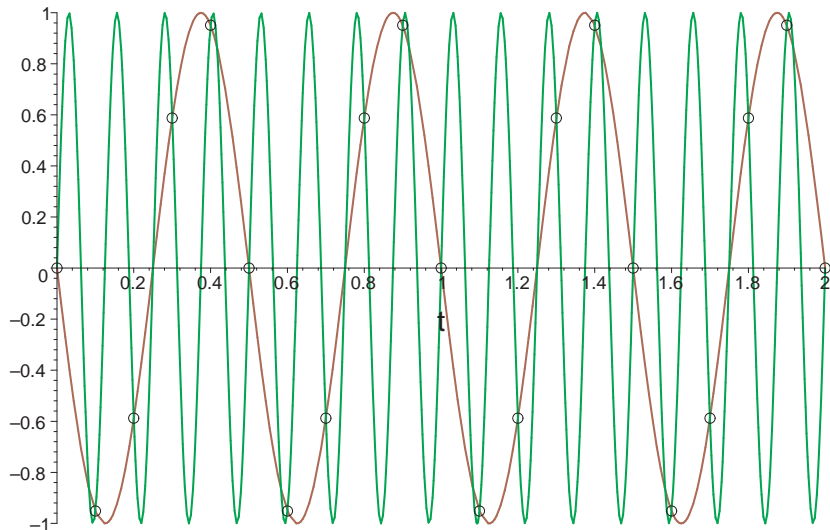

$f_c = 10$ , resp.  $f_c/2 = 5$

$\sin(2\pi 8t)$ , resp.  $-\sin(2\pi 2t)$


# Sampling of analog signals

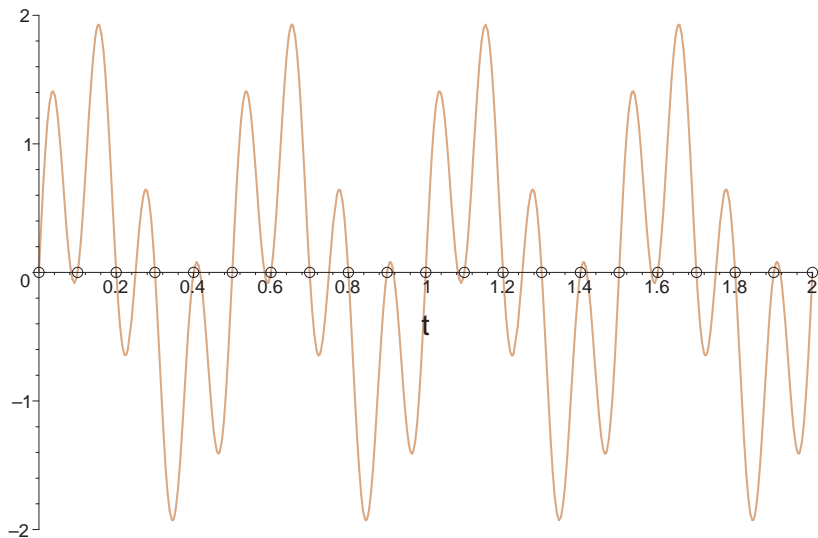


$f_c = 10$ , resp.  $f_c/2 = 5$

$$\sin(2\pi 2t) + \sin(2\pi 8t)$$
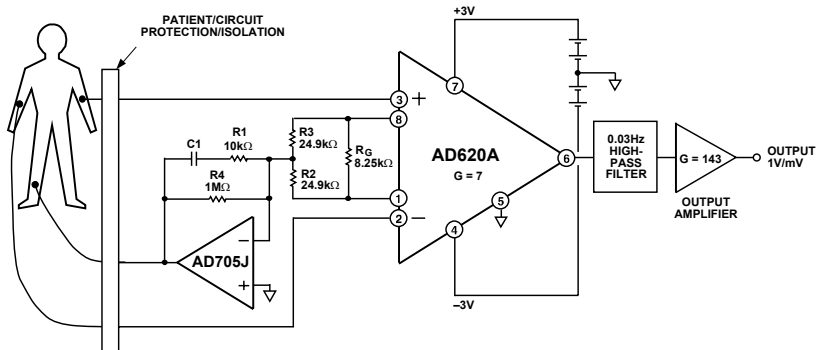
## Amplifier for Electrocardiograph (ECG) sensing


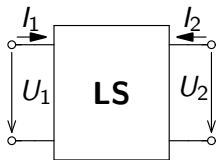
## Transfer characteristics of the linear systems




$$U_1(s) = \mathcal{L}\{u_1(t)\}, \quad U_2(s) = \mathcal{L}\{u_2(t)\},$$

$$i_1(s) = \mathcal{L}\{i_1(t)\}, \quad i_2(s) = \mathcal{L}\{i_2(t)\}.$$

$$\begin{bmatrix} i_1 \\ i_2 \\ 0 \\ \vdots \\ 0 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} & y_{13} & \cdots & y_{1n} \\ y_{21} & y_{22} & y_{23} & \cdots & y_{2n} \\ y_{31} & y_{32} & y_{33} & \cdots & y_{3n} \\ \vdots & \vdots & \vdots & \ddots & \vdots \\ y_{n1} & y_{n2} & y_{n3} & \cdots & y_{nn} \end{bmatrix} \begin{bmatrix} U_1 \\ U_2 \\ U_3 \\ \vdots \\ U_n \end{bmatrix} \equiv \mathbf{I} = \mathbf{Y} \mathbf{U}$$
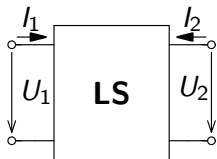
## Transfer characteristics of the linear systems



$$U_1(s) = \mathcal{L}\{u_1(t)\}, \quad U_2(s) = \mathcal{L}\{u_2(t)\},$$

$$I_1(s) = \mathcal{L}\{i_1(t)\}, \quad I_2(s) = \mathcal{L}\{i_2(t)\}.$$


$$\mathbf{I} = \mathbf{Y} \mathbf{U} \Rightarrow U_k = \frac{1}{|\mathbf{Y}|} \sum_{i=1}^n |\mathbf{Y}|_{ik} I_i,$$

two-port description we get for reduction  $k = 1, 2$ , and  $i = 1, 2$ :

$$U_1 = \frac{|\mathbf{Y}|_{11}}{|\mathbf{Y}|} I_1 + \frac{|\mathbf{Y}|_{21}}{|\mathbf{Y}|} I_2 = z_{11} I_1 + z_{12} I_2,$$

$$U_2 = \frac{|\mathbf{Y}|_{12}}{|\mathbf{Y}|} I_1 + \frac{|\mathbf{Y}|_{22}}{|\mathbf{Y}|} I_2 = z_{21} I_1 + z_{22} I_2.$$
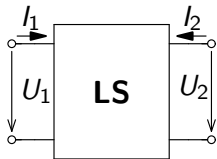
## Transfer characteristics of the linear systems



$$U_1(s) = \mathcal{L}\{u_1(t)\}, \quad U_2(s) = \mathcal{L}\{u_2(t)\},$$

$$I_1(s) = \mathcal{L}\{i_1(t)\}, \quad I_2(s) = \mathcal{L}\{i_2(t)\}.$$

## Impedance parameters (z-parameters)


$$\begin{bmatrix} U_1 \\ U_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$z_{11} = \left. \frac{U_1}{I_1} \right|_{I_2=0}, \quad z_{12} = \left. \frac{U_1}{I_2} \right|_{I_1=0},$$

$$z_{21} = \left. \frac{U_2}{I_1} \right|_{I_2=0}, \quad z_{22} = \left. \frac{U_2}{I_2} \right|_{I_1=0},$$

For reciprocal networks  $z_{12} = z_{21}$ . For symmetrical networks  $z_{11} = z_{22}$ . For lossless networks all the  $z_{mn}$  are purely imaginary.
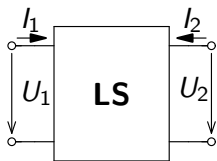
## Transfer characteristics of the linear systems



$$U_1(s) = \mathcal{L}\{u_1(t)\}, \quad U_2(s) = \mathcal{L}\{u_2(t)\},$$

$$I_1(s) = \mathcal{L}\{i_1(t)\}, \quad I_2(s) = \mathcal{L}\{i_2(t)\}.$$

## Admittance parameters (y-parameters)

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} U_1 \\ U_2 \end{bmatrix}$$


$$y_{11} = \left. \frac{I_1}{U_1} \right|_{U_2=0}, \quad y_{12} = \left. \frac{I_1}{U_2} \right|_{U_1=0},$$

$$y_{21} = \left. \frac{I_2}{U_1} \right|_{U_2=0}, \quad y_{22} = \left. \frac{I_2}{U_2} \right|_{U_1=0},$$

For reciprocal networks  $y_{12} = y_{21}$ . For symmetrical networks  $y_{11} = y_{22}$ . For lossless networks all the  $z_{mn}$  are purely imaginary ( $\mathbf{Z} = \mathbf{Y}^{-1}$ ).


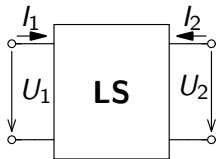
## Transfer characteristics of the linear systems



$$U_1(s) = \mathcal{L}\{u_1(t)\}, \quad U_2(s) = \mathcal{L}\{u_2(t)\},$$

$$I_1(s) = \mathcal{L}\{i_1(t)\}, \quad I_2(s) = \mathcal{L}\{i_2(t)\}.$$


## Hybrid parameters (h-parameters)

$$\begin{bmatrix} U_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ U_2 \end{bmatrix}$$

$$h_{11} = \left. \frac{U_1}{I_1} \right|_{U_2=0}, \quad h_{12} = \left. \frac{U_1}{U_2} \right|_{I_1=0},$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{U_2=0}, \quad h_{22} = \left. \frac{I_2}{U_2} \right|_{I_1=0},$$
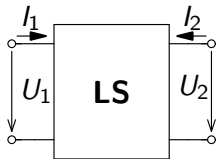
## Transfer characteristics of the linear systems



$$U_1(s) = \mathcal{L}\{u_1(t)\}, \quad U_2(s) = \mathcal{L}\{u_2(t)\},$$

$$i_1(s) = \mathcal{L}\{i_1(t)\}, \quad i_2(s) = \mathcal{L}\{i_2(t)\}.$$

## Cascade (chain, or transmission line) parameters (a-parameters)


$$\begin{bmatrix} U_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} U_2 \\ -i_2 \end{bmatrix}$$

$$a_{11} = \left. \frac{U_1}{U_2} \right|_{i_2=0}, \quad a_{12} = \left. \frac{U_1}{-i_2} \right|_{U_2=0},$$

$$a_{21} = \left. \frac{i_1}{U_2} \right|_{i_2=0}, \quad a_{22} = \left. \frac{i_1}{-i_2} \right|_{U_2=0},$$


For reciprocal networks  $a_{11}a_{22} - a_{12}a_{21} = 1$ . For symmetrical networks  $a_{11} = a_{22}$ . For networks which are reciprocal and lossless,  $a_{11}$  and  $a_{22}$  are purely real while  $a_{12}$  and  $a_{21}$  are purely imaginary. ▶
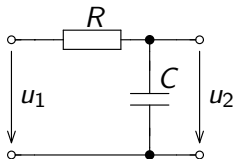
## Description and transfer characteristics of the RC network





$$H_{RC}(s) = \frac{U_2(s)}{U_1(s)} = \frac{H_0}{1 + sRC}$$

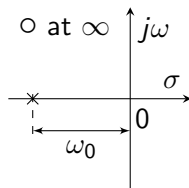
$$H_0 = 1, \quad \omega_0 = 2\pi f_0 = \frac{1}{RC}$$



$$s = j\omega \Rightarrow$$

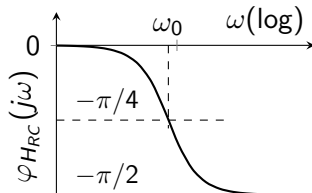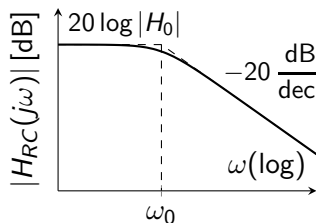

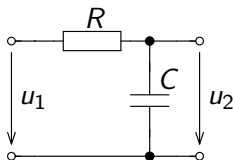
## Description and transfer characteristics of the RC network



$$H_{RC}(s) = \frac{U_2(s)}{U_1(s)} = \frac{H_0 \omega_0}{s + \omega_0}$$
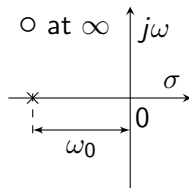
$$H_0 = 1, \quad \omega_0 = 2\pi f_0 = \frac{1}{RC}$$





$$h(t) = \mathcal{L}^{-1}\{H(s) \cdot 1\}$$


$$w(t) = \mathcal{L}^{-1}\{H(s)/s\}$$

$$h(t) = \frac{dw(t)}{dt}$$

$$w(t) = \int_0^t h(\tau) d\tau.$$

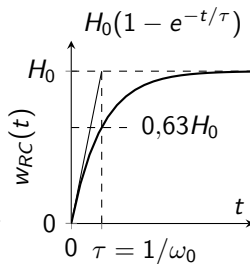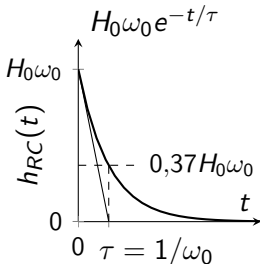
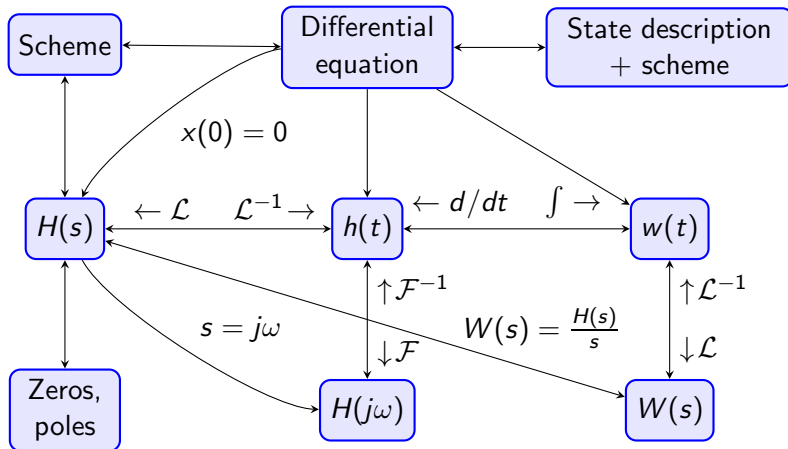
## Transfer characteristics of the linear systems



## Laplace transform Definition

$$F(s) = \mathcal{L}\{f(t)\} = \int_0^{\infty} f(t)e^{-st} dt$$

## Properties











Linearity	$af(t) + bg(t)$	$F(s) + bG(s)$
Differentiation	$\frac{df(t)}{dt}$	$sF(s) - f(0^-)$
Integration	$\int_0^t f(\tau) d\tau = \mathbf{1}(t) * f(t)$	$\frac{1}{s}F(s)$
Convolution	$(f * g)(t) = \int_0^t f(\tau)g(t - \tau) d\tau$	$F(s) \cdot G(s)$
Damping	$e^{at}f(t)$	$F(s - a)$
Time scaling	$f(at)$	$1/a F(s/a)$
Time shifting	$f(t - a)$	$e^{-as}F(s)$
Initial value	$f(0^+) = \lim_{s \rightarrow \infty} sF(s)$	
Final value	$f(\infty) = \lim_{s \rightarrow 0} sF(s); \quad \lim_{s \rightarrow 0} s \frac{1}{s} H(s) = H(0) = \text{DCgain}$	

## Table of selected Laplace transforms

Function	Time domain	Laplace s-domain
Unit impulse	$\delta(t)$	1
Unit step	$\mathbf{1}(t)$	$\frac{1}{s}$
Delayed unit step	$\mathbf{1}(t - \tau)$	$e^{-\tau s} \frac{1}{s}$
ramp	$t \cdot \mathbf{1}(t)$	$\frac{1}{s^2}$
exponential decay	$e^{-\alpha t} \cdot \mathbf{1}(t)$	$\frac{1}{s + \alpha}$
exponential approach	$(1 - e^{-\alpha t}) \cdot \mathbf{1}(t)$	$\frac{\alpha}{s(s + \alpha)} = \frac{1}{s} - \frac{\alpha}{s + \alpha}$
sine	$\sin(\omega t) \cdot \mathbf{1}(t)$	$\frac{\omega}{s^2 + \omega^2}$
cosine	$\cos(\omega t) \cdot \mathbf{1}(t)$	$\frac{s}{s^2 + \omega^2}$

see more, e.g. [http://en.wikipedia.org/wiki/Laplace\\_transform](http://en.wikipedia.org/wiki/Laplace_transform)

# Dynamic System Description

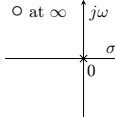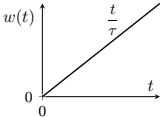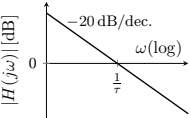
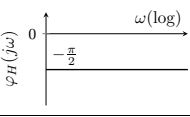
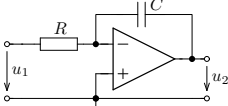
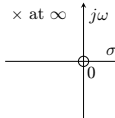
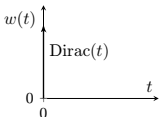
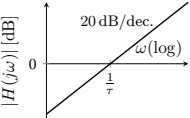
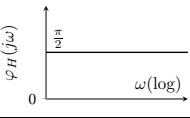
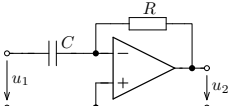
Transfer function	Poles, Zeros, Unit step response	Module and phase frequency response	Passive and active circuit realization
<p>Ideal integrator</p> $H(s) = \frac{1}{s\tau}$	 	 	<p>Realization by passive circuit does not exist.</p> <hr/> <p>Inverting integrator</p>  $H(s) = -\frac{1}{s\tau}, \tau = \frac{1}{RC}$
<p>Ideal derivator</p> $H(s) = s\tau$	 	 	<p>Realization by passive circuit does not exist.</p> <hr/> <p>Inverting derivator</p>  $H(s) = -s\tau, \tau = \frac{1}{RC}$



# Dynamic System Description

Transfer function	Poles, Zeros, Unit step response	Module and phase frequency response	Passive and active circuit realization
<p>Low pass (LP<sub>1</sub>)</p> $H(s) = \frac{H_0 \omega_0}{s + \omega_0}$ <p><math>\omega_0 &gt; 0, H_\infty = 0</math></p>			<p><math>\omega_0 = \frac{1}{RC}, H_0 = 1</math></p> <p><math>\omega_0 = \frac{1}{R_2 C}, H_0 = -\frac{R_2}{R_1}</math></p>
<p>High pass (HP<sub>1</sub>)</p> $H(s) = \frac{H_\infty s}{s + \omega_0}$ <p><math>\omega_0 &gt; 0, H_0 = 0</math></p>			<p><math>\omega_0 = \frac{1}{RC}, H_\infty = 1</math></p> <p><math>\omega_0 = \frac{1}{R_1 C}, H_\infty = -\frac{R_2}{R_1}</math></p>

# Dynamic System Description

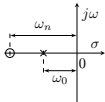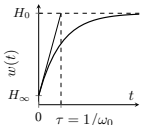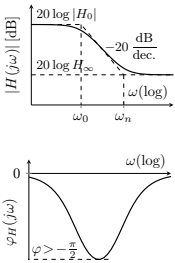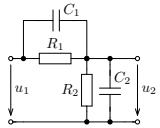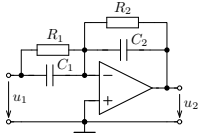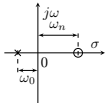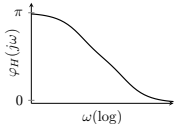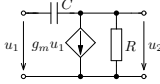Transfer function	Poles, Zeros, Unit step response	Module and phase frequency response	Passive and active circuit realization
$H(s) = H_{\infty} \frac{s + \omega_n}{s + \omega_0}$ $\omega_0 > 0, \omega_n > 0$	  $H_0 = H_{\infty} \frac{\omega_n}{\omega_0}$		 $\omega_0 = \frac{1}{(R_1    R_2)(C_1 + C_2)},$ $\omega_n = \frac{1}{R_1 C_1}, H_0 = \frac{R_2}{R_1 + R_2},$ $H_{\infty} = \frac{C_1}{C_1 + C_2},$  $\omega_0 = \frac{1}{R_2 C_2}, \omega_n = \frac{1}{R_1 C_1},$ $H_0 = -\frac{R_2}{R_1}, H_{\infty} = -\frac{C_1}{C_2}.$
$H(s) = H_{\infty} \frac{s - \omega_n}{s + \omega_0}$ $\omega_0 > 0, \omega_n > 0$	 <p>step resp. is the same</p> $H_0 = -H_{\infty} \frac{\omega_n}{\omega_0}$	<p>module resp. is the same</p> 	 $\omega_0 = \frac{1}{RC}, \omega_n = \frac{g_m}{C},$ $H_0 = -\frac{g_m}{R}, H_{\infty} = 1.$






Transfer function	Poles, Zeros, Unit step response	Module and phase frequency response	Passive and active circuit realization
<p>All pass (AP<sub>1</sub>)</p> $H(s) = H_{\infty} \frac{s - \omega_0}{s + \omega_0}$ <p><math>\omega_0 &gt; 0, \omega_n &gt; 0</math></p>	 <p><math>H_0 = -H_{\infty}</math></p>		 <p><math>\omega_0 = \frac{1}{RC}, H_0 = 1/2,</math></p> <p><math>\omega_0 = \frac{1}{RC}, H_0 = 1.</math></p>

Table: First-order all-pass section.


## Frequency response of the one RC network, $f_0 = 10 \text{ kHz}$


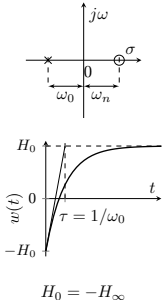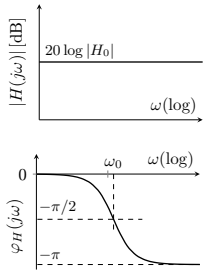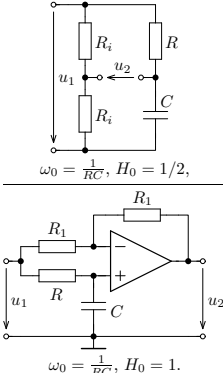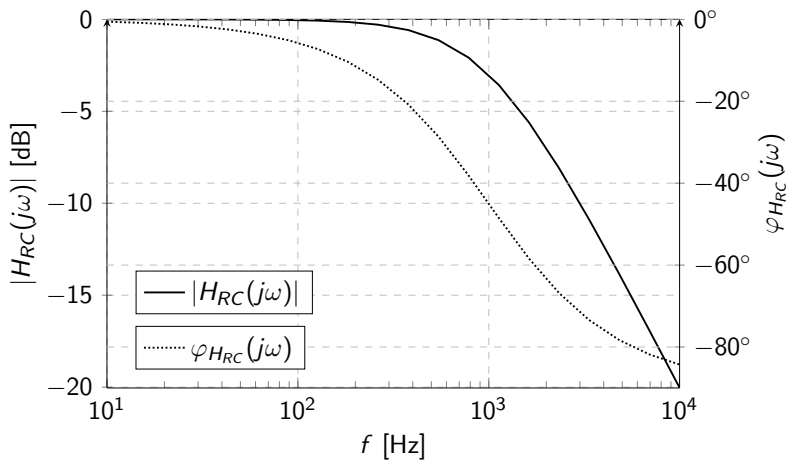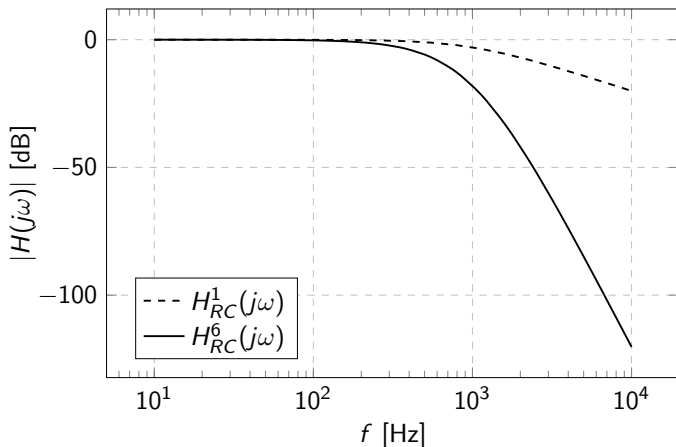
## Module frequency response of the one and six RC networks


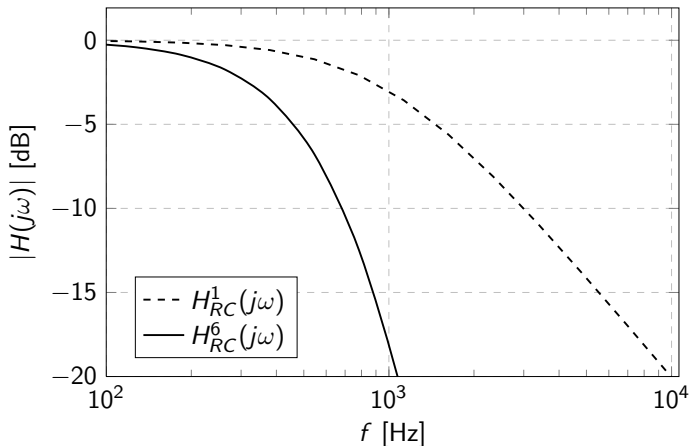
## Module frequency response of the one and six RC networks




## Cascade structure of the filter – cascading transfer function

$$H(s) = \frac{s^m + a_{m-1}s^{m-1} + \dots + a_0}{b_ns^n + b_{n-1}s^{n-1} + \dots + b_0} = H_\infty \frac{(s - s_{n1})(s - s_{n2}) \dots (s - s_{nm})}{(s - s_{p1})(s - s_{p2}) \dots (s - s_{pm})},$$

where  $s_{p_i} = \sigma_{p_i} \pm j\omega_{p_i}$ , and  $\omega_{0_i} = |s_{p_i}| = \sqrt{\omega_{p_i}^2 + \sigma_{p_i}^2}$ ,  $Q_i = \frac{1}{2} \frac{\omega_{0_i}}{|\sigma_{p_i}|} = \frac{1}{2\xi}$ ,

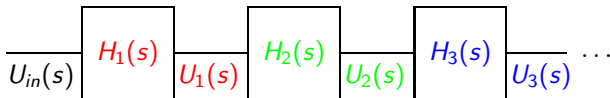general 2<sup>nd</sup> order TF  $H_b(s) = H_\infty \frac{(s - \omega_n)^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$ .



transfer function of the block  $k$ :  $H_k(s) = \frac{U_k(s)}{U_{k-1}(s)}$ ,

transfer function after the block  $k$ :  $H_{1 \rightarrow k}(s) = \frac{U_k(s)}{U_{in}(s)} = \prod_{n=1}^k H_n(s)$ .

## Time response of the 2<sup>nd</sup> order (biquadratic) transfer function – biquad

$$H(s) = \frac{C(s - s_{n1})}{(s - s_{p1})(s - s_{p2})} \xrightarrow{\mathcal{L}^{-1}} h(t) = C_1 e^{s_{p1}t} + C_2 e^{s_{p2}t},$$

$$H(s) = \frac{C}{(s - s_{p1})(s - s_{p2})} \xrightarrow{\mathcal{L}^{-1}} h(t) = \left|_{s_{p12} = \sigma_p \pm j\omega_p} \frac{C}{\omega_p} e^{\sigma_p t} \sin(t\omega_p), \right.$$

$$H_{LP}(s) = \frac{H_0 \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} \quad \forall \sigma_p < 0$$

$$\text{where poles are } s_{p12} = \frac{(-1 \pm \sqrt{1 - 4Q^2}) \omega_0}{2Q},$$

where  $Q = \frac{1}{2\xi}$  – quality factor of the biquad and  
 $\xi = \frac{1}{2Q}$  – damping factor.



## Frequency Filters – effect of the pole position on the type of responses



$$H_{LP}(s) = \frac{H_0 \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} \quad \forall \sigma_p < 0, \quad \text{where} \quad s_{p12} = \frac{(-1 \pm \sqrt{1 - 4Q^2}) \omega_0}{2Q},$$

$Q < 1/2$ ,  $\xi > 1$  two real poles,


$Q = 1/2$ ,  $\xi = 1$  double real pole,

$Q > 1/2$ ,  $\xi < 1$  complex conjugate poles, where special case

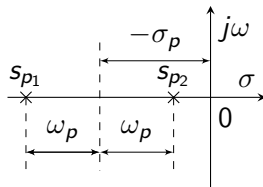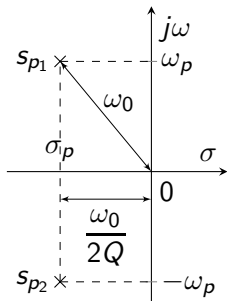$Q = \xi = 1/\sqrt{2}$  – complex conjugate poles with  $\sigma_p = \omega_p$ .



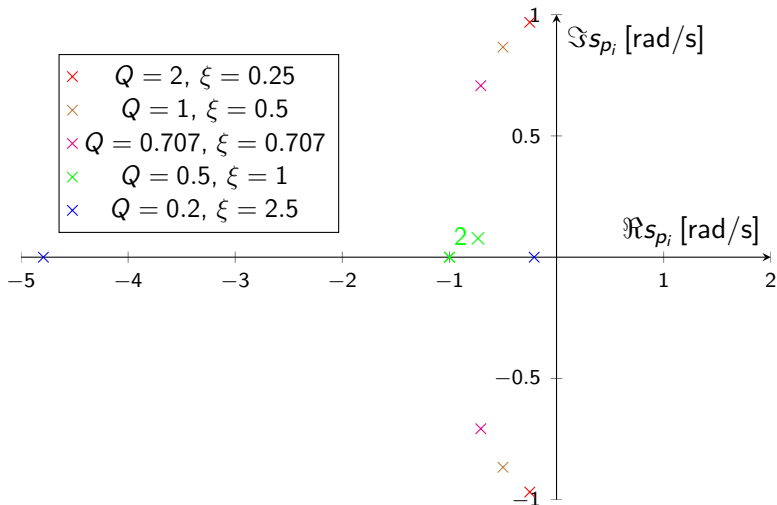
## Poles location of the biquad for $\omega_0 = 1$




## Magnitude frequency responses of the biquad for


$$H_0 = H_{LP}(0) = 1$$

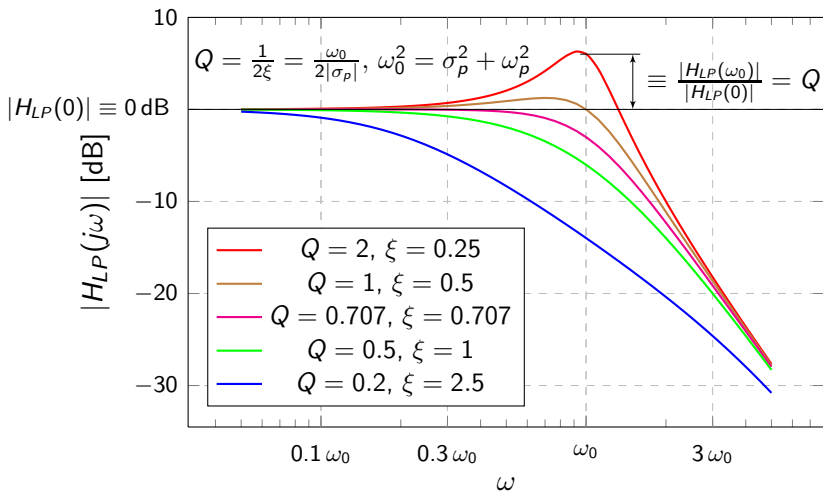

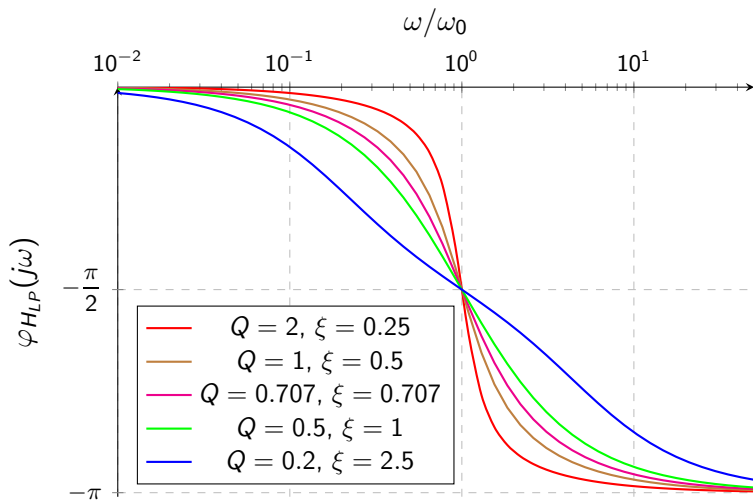
## Phase frequency responses of the biquad



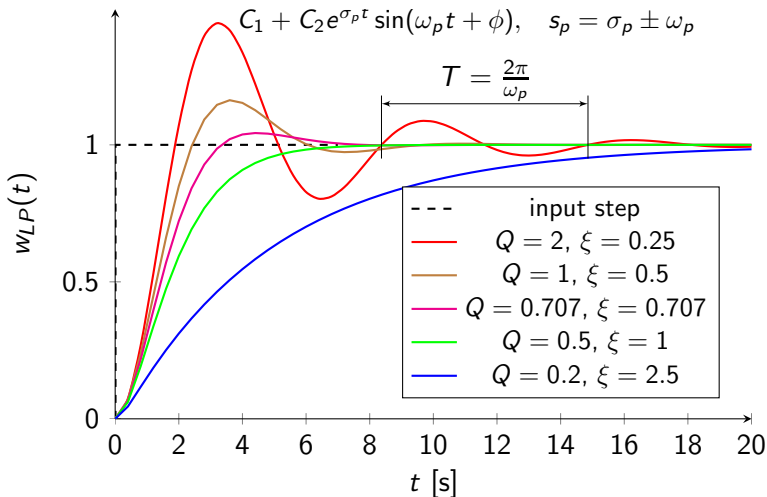
**Time (unit step) responses of the biquad for  $H_0 = 1$  and  $\omega_0 = 1$**



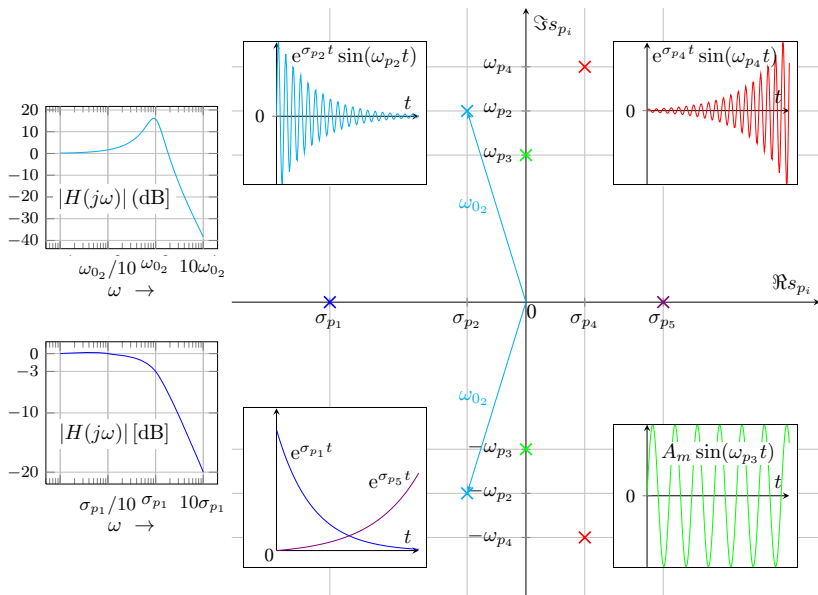
# Frequency Filters – effect of the pole position on the type of responses


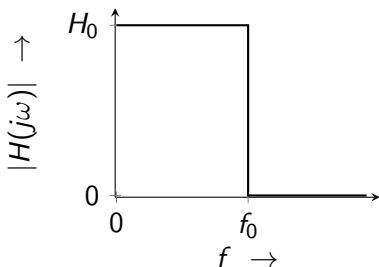
## Magnitude Specification of the Ideal and Real Lowpass (LP) Filter




**Ideal LP filter** ( $f_p = f_s = f_0$ )  
 passband  $\equiv \langle 0, f_0 \rangle$ ,  $|H| = H_0$ ,  
 transition band  $\equiv 0$ ,  
 stopband  $\equiv \langle f_0, \infty \rangle$ ,  $|H| = 0$


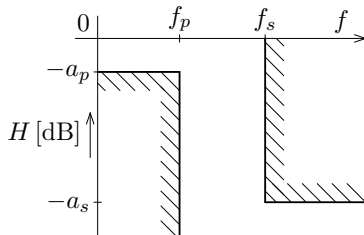


**Real LP filter**  
 passband  $\equiv \langle 0, f_p \rangle$ ,  $|H| = \langle H_0, H_0 - a_p \rangle$ ,  
 transition band  $\equiv (f_p, f_s)$ ,  
 stopband  $\equiv \langle f_s, \infty \rangle$ ,  $|H| < H_0 - a_s$

# Frequency Filters

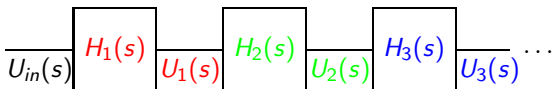


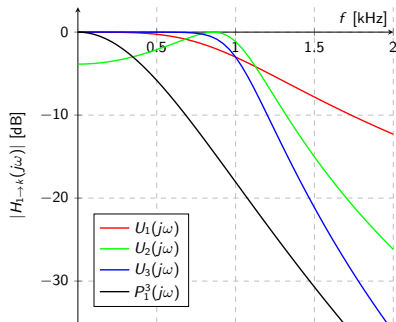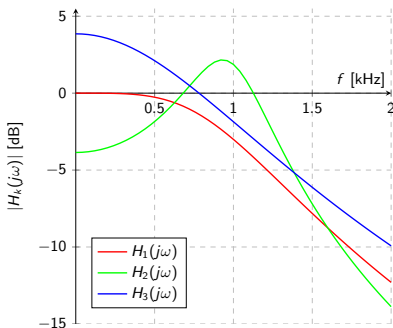Butterworth filter  $f_{01} = 1 \text{ kHz}, \quad f_{02} = 1 \text{ kHz}, \quad f_{03} = 1 \text{ kHz},$   
 $Q_1 = 0.71, \quad Q_2 = 1.9, \quad Q_3 = 0.52.$








# Frequency Filters

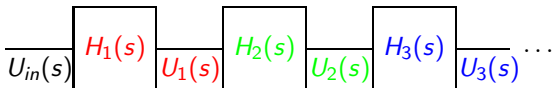

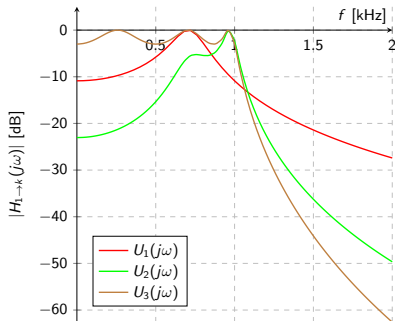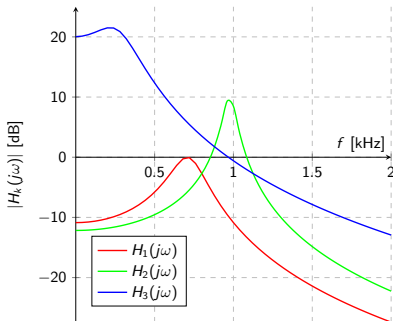Chebyshev filter       $f_{01} = 0.7 \text{ kHz}$ ,       $f_{02} = 0.96 \text{ kHz}$ ,       $f_{03} = 0.3 \text{ kHz}$ ,  
                                  $Q_1 = 3.5$ ,                       $Q_2 = 13$ ,                       $Q_3 = 1$ .





# Frequency Filters

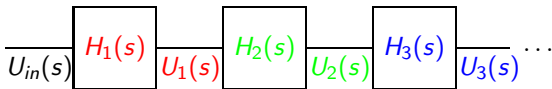


Cauer filter


$f_{01} = 0.77 \text{ kHz},$	$f_{02} = 0.99 \text{ kHz},$	$f_{03} = 0.32 \text{ kHz},$
$f_{n1} = 2.7 \text{ kHz},$	$f_{n2} = 2.1 \text{ kHz},$	$f_{03} = 7 \text{ kHz},$
$Q_1 = 3.7,$	$Q_2 = 15,$	$Q_3 = 1.1.$

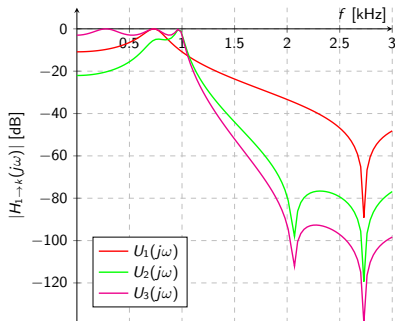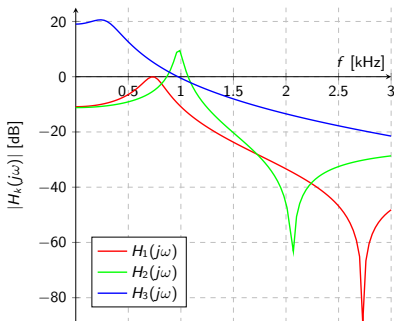

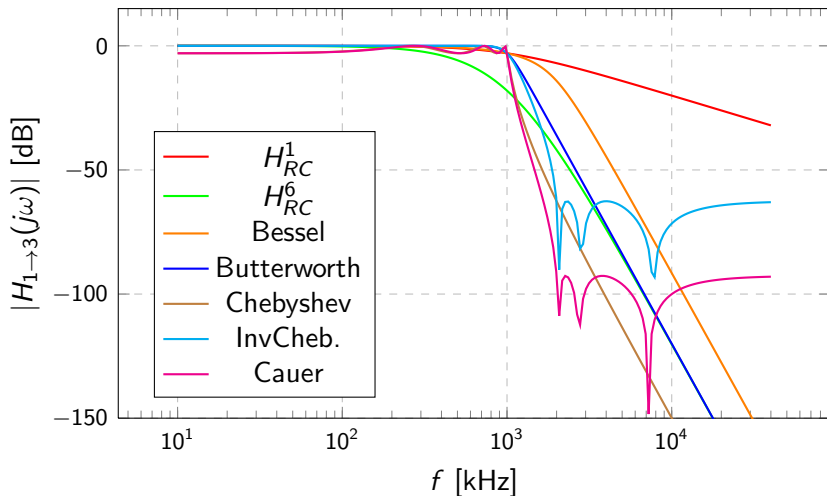
## Magnitude frequency responses of the filters



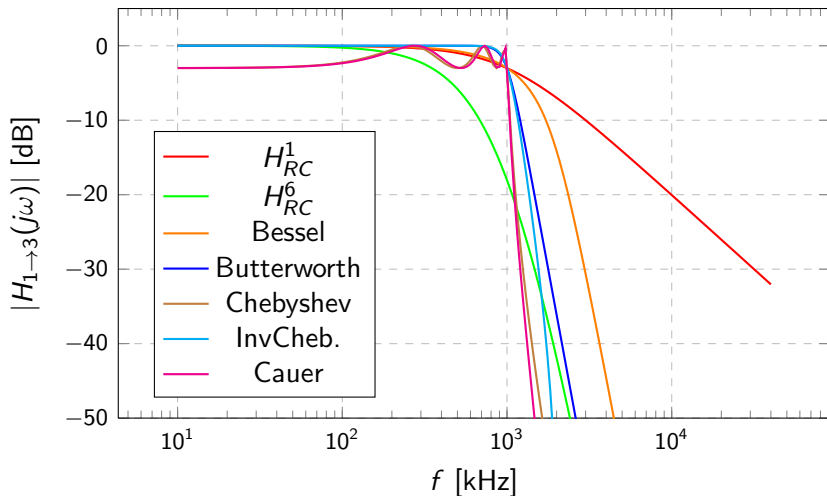
## Magnitude frequency responses of the filters



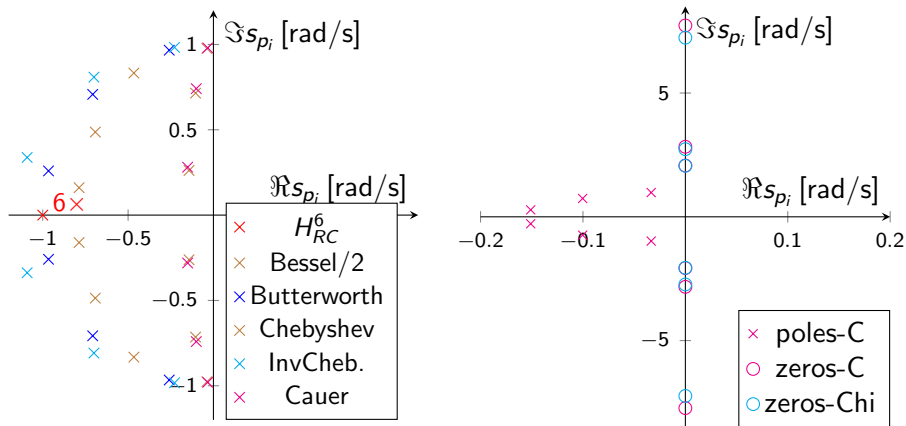
**Poles of the filters, poles and zeros of the Cauer and Inverse Chebyshev filter in  $p$ -plane for normalized frequency  $\omega_0 = 1$ .**



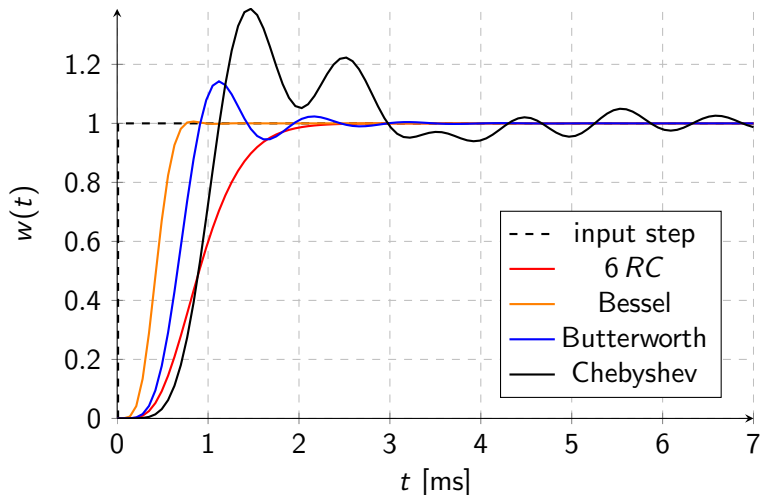**Time (unit step) responses of the filters** (Phase- and Amplitude errors cause linear distortions)


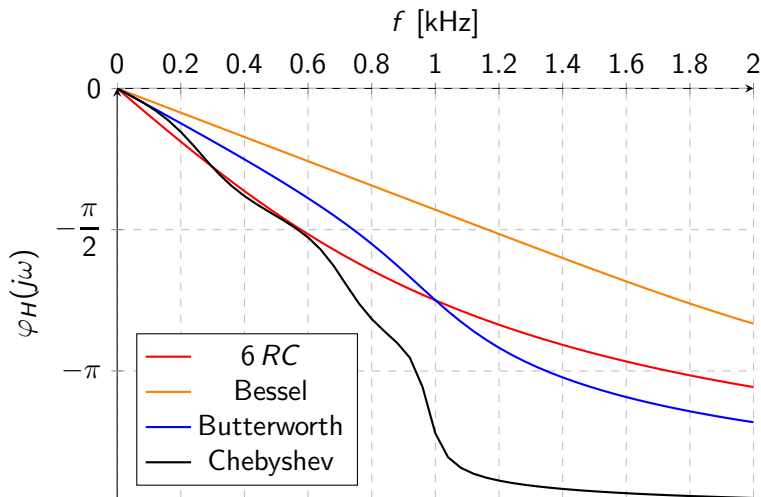
## Phase frequency responses of the filters



## Why do we need a good time response?

Filter for DC value of rectifier signal, ...


## Why the phase frequency responses should be linear (not constant)?

Phase values of sinusoidal waveform for delay e.g.  $\tau = 1/2$  ms.


$f$ [kHz]	$T$ [ms]	$\tau = 1/2$ ms
1	1	$T/2 \equiv 1\pi$
2	1/2	$1T \equiv 2\pi$
6	1/6	$3T \equiv 6\pi$



## Group delays of the filters

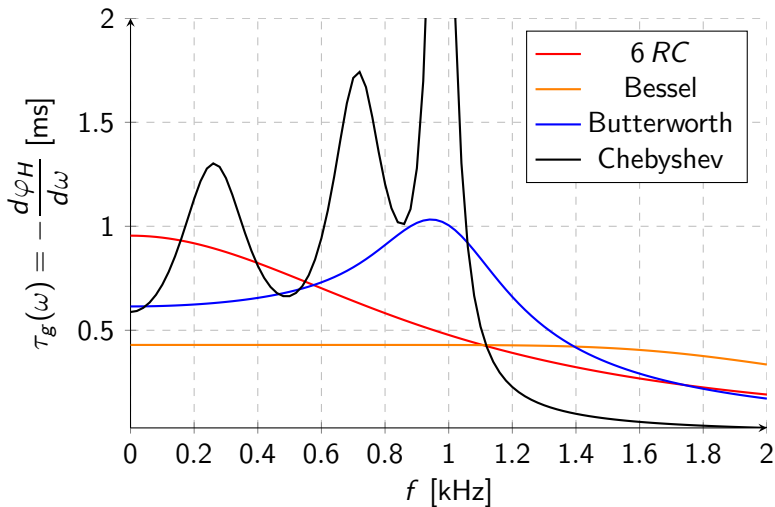


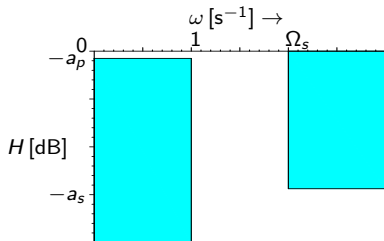Frequency transformations, normalization, solving of approximation task, electric filter synthesis, analysis resulted structures.


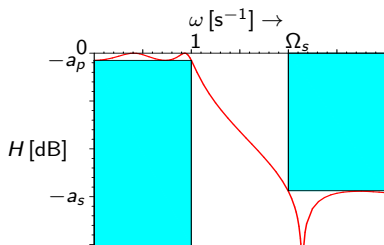
# Filter Design Steps


Frequency transformations, normalization, **solving of approximation task**, electric filter synthesis, analysis resulted structures.



$$\begin{aligned} \Rightarrow H(s) &= \frac{s^m + a_{m-1}s^{m-1} + \dots + a_0}{b_ns^n + b_{n-1}s^{n-1} + \dots + b_0} \\ \Leftarrow \end{aligned}$$

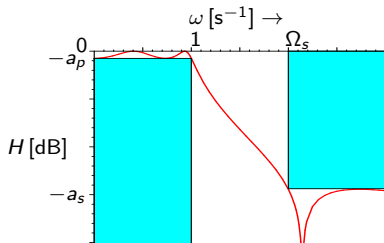
# Filter Design Steps

Frequency transformations, normalization, solving of approximation task, **electric filter synthesis**, analysis resulted structures.




$\Rightarrow$   
 $\Leftarrow$
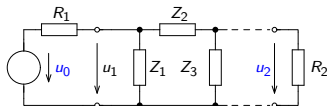
$$H(s) = \frac{s^m + a_{m-1}s^{m-1} + \dots + a_0}{b_ns^n + b_{n-1}s^{n-1} + \dots + b_0}$$


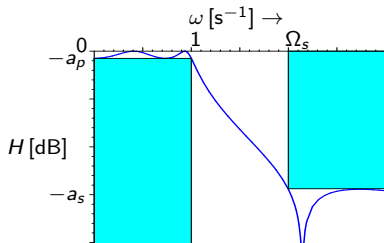
# Filter Design Steps


Frequency transformations, normalization, solving of approximation task, electric filter synthesis, **analysis resulted structures.**



$\Rightarrow$

$$H(s) = \frac{s^m + a_{m-1}s^{m-1} + \dots + a_0}{b_n s^n + b_{n-1}s^{n-1} + \dots + b_0}$$


$\Leftarrow$

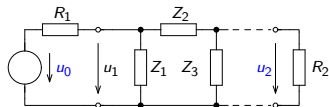


$\Leftarrow$

$$H(s) = \frac{U_2(s)}{U_0(s)} \left( \sqrt{\frac{4R_1}{R_2}} \right) = \sqrt{\frac{P_2}{P_{max}}}$$


# Frequency Transformations

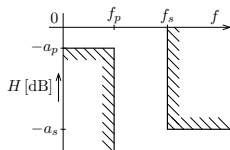


Lowpass

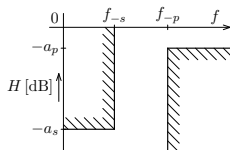


Highpass

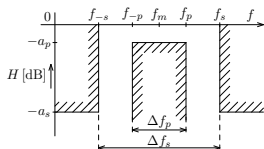

Bandpass

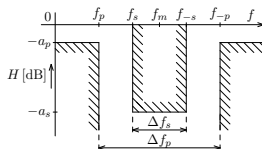



Band-stop

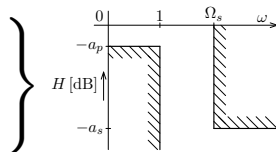



Normalized Lowpass

Filter Characteristic for Lowpass (LP), Highpass (HP), Bandpass (BP), Band-rejection (or Band-stop – BS) and Normalized Lowpass (NLP).

# Magnitude Approximation

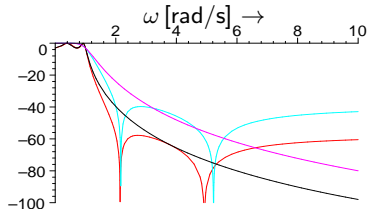
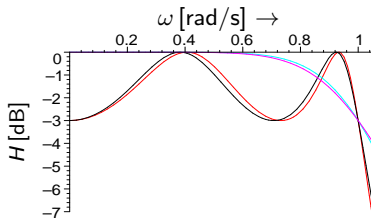


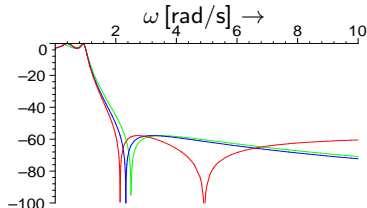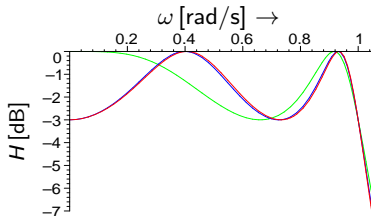Butterworth, Chebyshev, Inverse Chebyshev A type and Cauer (A),





Cauer A, B and C type approximation of NLP filter magnitude

# Magnitude Approximation

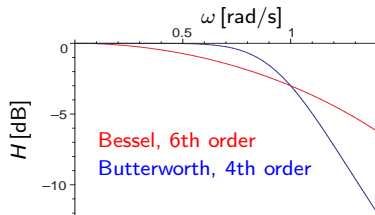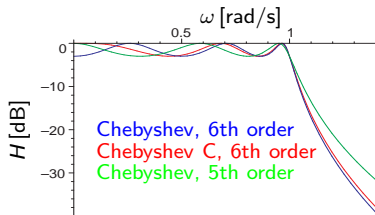

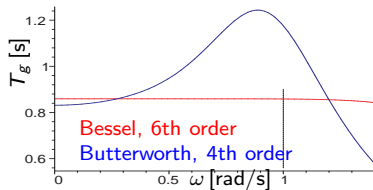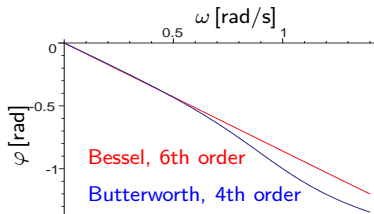Comparison of Chebyshev A vs C type and Butterworth vs Bessel approximation



Comparison of phase and group delay characteristic of Butterworth and Bessel approximation



## Results of Approximation Task

- secondary parameters of the filter (order, new stopband value, ...)
- zeros and poles of gain and characteristic function
- gain and characteristic function
- partial gain functions (parameters of biquads –  $\omega_0$ ,  $Q$ ,  $[\omega_n]$ ) appropriate for cascade filter synthesis

## Analog filters realization




### 1 Passive filters

- Electromechanical filters,  $10^1 \text{ kHz} < f < 10^2 \text{ kHz}$ ,
- LC filters,  $10^0 \text{ kHz} < f < 1 \text{ GHz}$ ,
- Crystal (piezoelectric) filters,  $10^1 \text{ kHz} < f < 1 \text{ GHz}$ ,
- Surface Acoustic Wave (SAW) filters,  $10 \text{ MHz} < f < 2 \text{ GHz}$ ,
- Microwave filter (cavity filters),  $f > 1 \text{ GHz}$ .





### 2 Active building blocks using

- Op Amps – ARC filters,
- OTA – transconductance amplifiers filters,
- Current conveyors (current-mode filters),
- Log-domain and Square-root domain filters,
- Discrete time filters using SC or SI technique.




## LC Filters

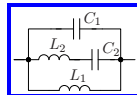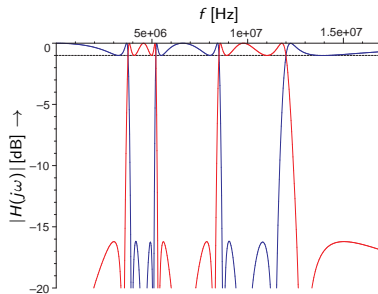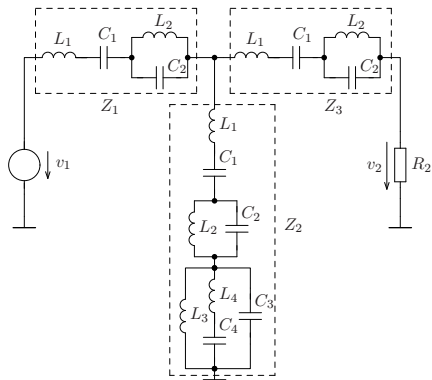

## LC Filters

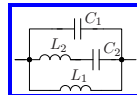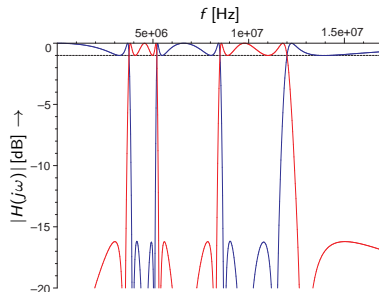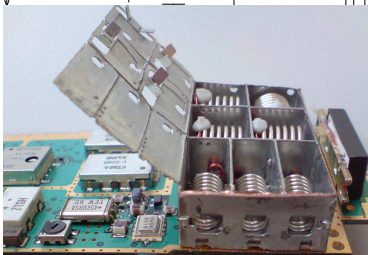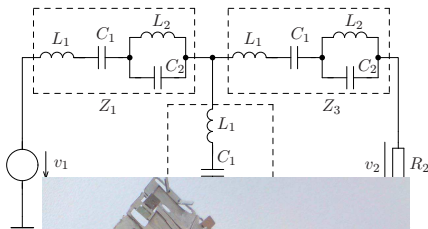


## LC Filters

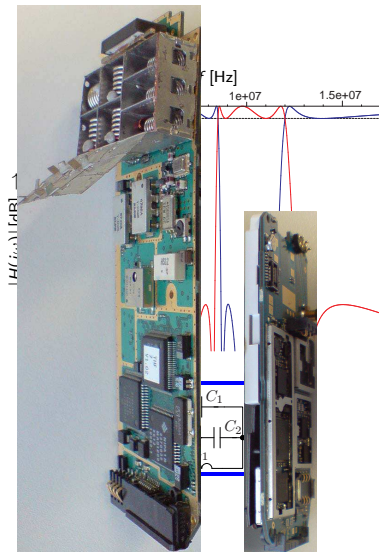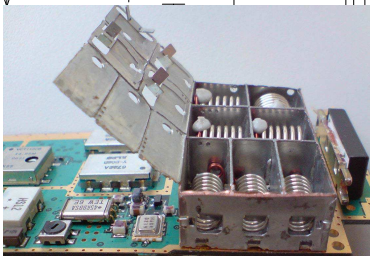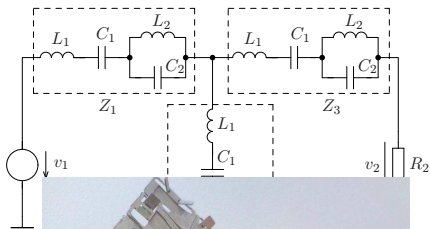

**ARC filters:** very good dynamic range at low frequencies, tuning is problem.

- LC ladder simulation by signal-flow graphs or by element substitution (synthetic inductors, Bruton's transformation),
- Cascade synthesis (forming biquadratic sections – biquads),
- Direct synthesis.
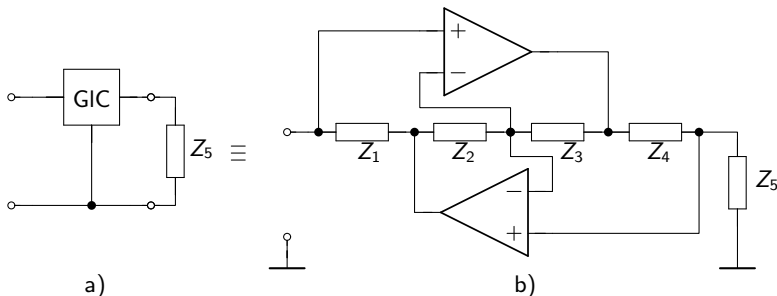
## Impedance converter and its realization



$$Z_{vst}(s) = k(s)Z_5 = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

**Inductor realization**  $Z_4 = 1/(sC)$  and  $Z_1 = Z_2 = Z_3 = Z_5 = R$ , then


$$Z_{vst}(p) = sCR^2$$

**Double capacitor realization**  $Z_1 = Z_3 = 1/(sC)$  and

$Z_2 = Z_4 = Z_5 = R$ , then


$$Z_{vst}(s) = \frac{1}{s^2 C^2 R}$$
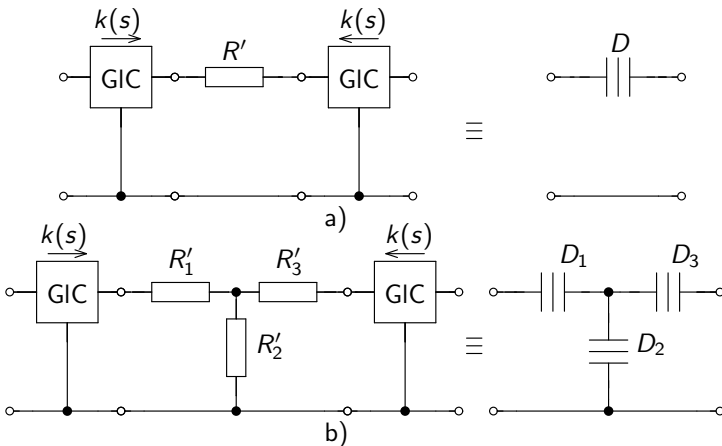
## Circuit realization of no-grounded double capacitor







## Circuit realization of LP filter

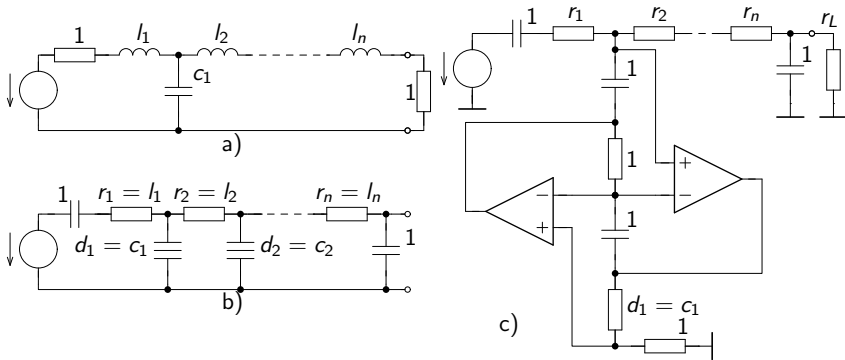


## Circuit realization of HP filter

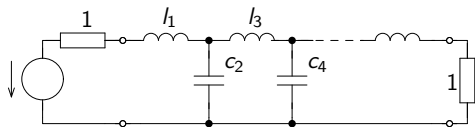


a)

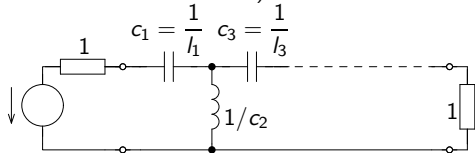

b)

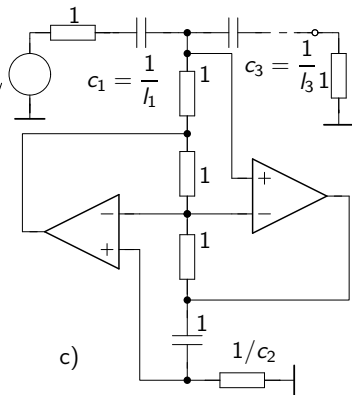

c)

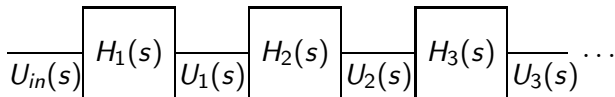

transfer function of the block  $k$ :  $H_k(s) = \frac{U_k(s)}{U_{k-1}(s)}$ ,

transfer function after the block  $k$ :  $H_{1 \rightarrow k}(s) = \frac{U_k(s)}{U_{in}(s)} = \prod_{n=1}^k H_n(s)$ .

Figure: Cascade structure of a filter.

# Cascade Filters

Transfer function	Poles, Zeros, Unit step response	Module and phase frequency response	Circuit realization
<p>Low pass (LP<sub>2</sub>)</p> $H(s) = \frac{H_0 \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$ <p><math>Q &gt; 0, \omega_0 &gt; 0,</math> <math>H_\infty = 0</math></p>	<p>Unit step response: <math>w(t)</math> (solid line), <math>g(e^{\sigma_p t})</math> (dotted line). Frequency <math>f = \frac{\omega_p}{2\pi}</math>.</p>	<p>Magnitude: <math> H(j\omega) </math> vs <math>\omega</math>. Peak at <math>\omega_0</math> with value <math>Q H_0 </math>. Phase: <math>\varphi_H(j\omega)</math> vs <math>\omega</math>. Starts at 0, ends at <math>-\pi</math>.</p>	<p><math>H_0 = 1,</math> <math>\omega_0 = \frac{1}{\sqrt{LC}}, Q = \omega_0 \frac{L}{R}</math></p> <p>active realization ⇒ see below</p>
<p>High pass (HP<sub>2</sub>)</p> $H(s) = \frac{H_\infty s^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$ <p><math>Q &gt; 0, \omega_0 &gt; 0,</math> <math>H_0 = 0</math></p>	<p>Unit step response: <math>w(t)</math> (solid line), <math>\pm H_\infty e^{\sigma_p t}</math> (dotted line). Frequency <math>f = \frac{\omega_p}{2\pi}</math>.</p>	<p>Magnitude: <math> H(j\omega) </math> vs <math>\omega</math>. Peak at <math>\omega_0</math> with value <math>Q H_\infty </math>. Phase: <math>\varphi_H(j\omega)</math> vs <math>\omega</math>. Starts at <math>\pi</math>, ends at 0.</p>	<p><math>H_\infty = 1,</math> <math>\omega_0 = \frac{1}{\sqrt{LC}}, Q = \omega_0 \frac{L}{R}</math></p> <p>active realization ⇒ see below</p>

# Cascade Filters

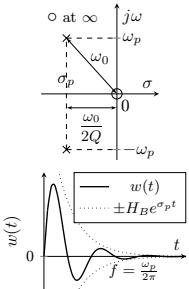
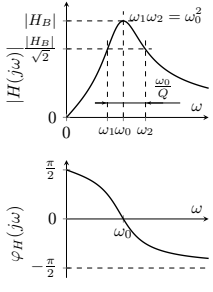
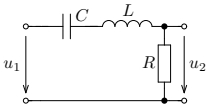
Transfer function	Poles, Zeros, Unit step response	Module and phase frequency response	Circuit realization
<p>Band pass (BP<sub>2</sub>)</p> $H(s) = \frac{H_B \frac{\omega_0}{Q} s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$ <p><math>Q &gt; 0, \omega_0 &gt; 0,</math> <math>H_0 = H_\infty = 0</math></p>			 <p> <math>H_B = 1,</math>  <math>\omega_0 = \frac{1}{\sqrt{LC}}, Q = \omega_0 \frac{L}{R}</math> </p> <hr/> <p>active realization ⇒ see below</p>

Table: Second-order filter section.

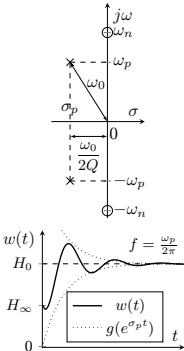
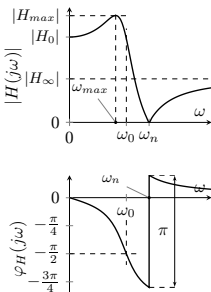
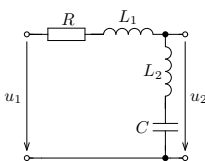
Transfer function	Poles, Zeros, Unit step response	Module and phase frequency response	Circuit realization
<p>Low pass notch (LPN)</p> $H(s) = \frac{H_0 \frac{\omega_n^2}{\omega_n^2} (s^2 + \omega_n^2)}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$ <p><math>\omega_n &gt; \omega_0 &gt; 0</math>, <math>Q &gt; 0</math></p>			 <p> <math>H_0 = 1</math>, <math>H_\infty = \frac{L_2}{L_1 + L_2}</math>,  <math>\omega_0 = \frac{1}{\sqrt{(L_1 + L_2)C}}</math>,  <math>\omega_n = \frac{1}{\sqrt{L_2 C}}</math>,  <math>Q = \omega_0 \frac{(L_1 + L_2)}{R}</math> </p> <p>active realization ⇒ see below</p>

Table: Second-order elliptic filter section.






Transfer function	Poles, Zeros, Unit step response	Module and phase frequency response	Circuit realization
<p>High pass notch (HPN)</p> $H(s) = \frac{H_\infty(s^2 + \omega_n^2)}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$ <p><math>\omega_0 &gt; \omega_n &gt; 0</math>, <math>Q &gt; 0</math></p>	 	 	 $H_\infty = 1, H_0 = \frac{C_1}{C_1 + C_2},$ $\omega_0 = \sqrt{\frac{C_1 + C_2}{C_1 C_2 L}},$ $\omega_n = \frac{1}{\sqrt{LC_2}}, Q = \omega_0 \frac{L}{R}$ <hr/> <p>active realization ⇒ see below</p>

Table: Second-order elliptic filter section.

# Cascade Filters





Transfer function	Poles, Zeros, Unit step response	Module and phase frequency response	Circuit realization
<p>Notch (N)</p> $H(s) = \frac{H_0(s^2 + \omega_0^2)}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$ <p><math>\omega_0 &gt; 0, Q &gt; 0</math>  <math>H_0 = H_\infty</math></p>			 <p> <math>H_0 = H_\infty = 1,</math>  <math>\omega_0 = \frac{1}{\sqrt{LC}},</math>  <math>Q = \omega_0 \frac{L}{R}</math> </p> <hr/> <p>active realization  <math>\Rightarrow</math> see below</p>

Table: Second-order elliptic filter section.

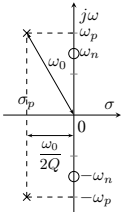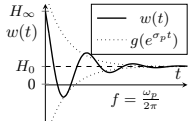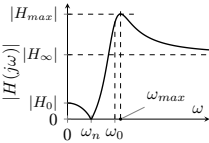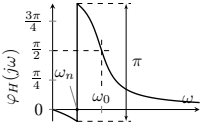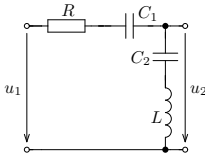

# Cascade Filters


Transfer function	Poles, Zeros, Unit step response	Module and phase frequency response	Circuit realization
<p>All pass (AP<sub>2</sub>)</p> $H(s) = \frac{s^2 - \frac{\omega_0}{Q}s + \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} = H_0 \frac{s^2 - \frac{\omega_0}{Q}s + \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$ <p><math>\omega_0 &gt; 0, Q &gt; 0</math>  <math>H_0 = H_\infty</math></p>			$H_0 = H_\infty = 1,$ $C = \frac{Q}{\omega_0 R}, C_2 = \frac{2Q}{\omega_0 R(Q^2 - 1)},$ $L_1 = \frac{2R}{\omega_0 Q}, L_2 = \frac{QR}{2\omega_0}$ <hr/> <p>active realization  <math>\Rightarrow</math> see below</p>

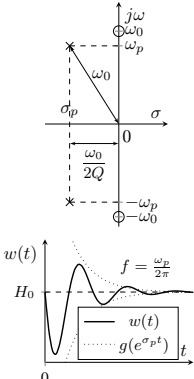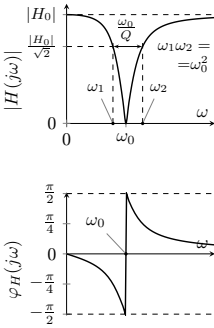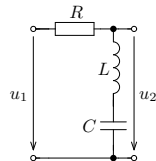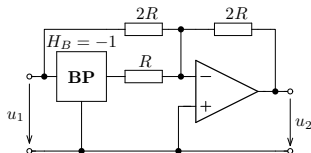

$$H(s) = \frac{U_2(s)}{U_1(s)} = \left( \frac{-2\frac{\omega_0}{Q}s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} + 1 \right) = -\frac{s^2 - \frac{\omega_0}{Q}s + \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

- Assignment particular zeros to corresponding poles, so-called pole-zero pairing to biquadratic functions are formed,
- determination of order in which the biquadratic functions (biquads) should be cascaded,
- choosing optimum gain distribution to particular biquads and
- electric circuit synthesis of particular biquad (choosing of appropriate circuit and element values calculation).
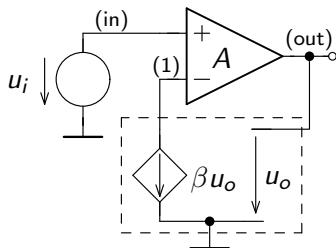
## Frequency Response of the Feedback Structure



$$H(s) = \frac{U_o(s)}{U_i(s)} = \frac{A(s)}{A(s)\beta + 1}$$

$$H(0) \doteq \frac{1}{\beta} \quad \forall \quad A(0)\beta \gg 1$$


$$1 \quad H_1(s) = \frac{A_0}{(1 + s/\omega_1)(1 + s/\omega_2)},$$

$$\text{where } A_0 = 10^5, \omega_1 = 2\pi 100, \omega_2 = 2\pi 2 \cdot 10^6$$

$$2 \quad H_2(s) = \frac{A_0}{(1 + s/\omega_1)(1 + s/\omega_2)(1 + s/\omega_3)},$$

$$\text{where } A_0 = 10^5, \omega_1 = 2\pi 100, \omega_2 = 2\pi 2 \cdot 10^6, \omega_3 = 2\pi 4 \cdot 10^6$$

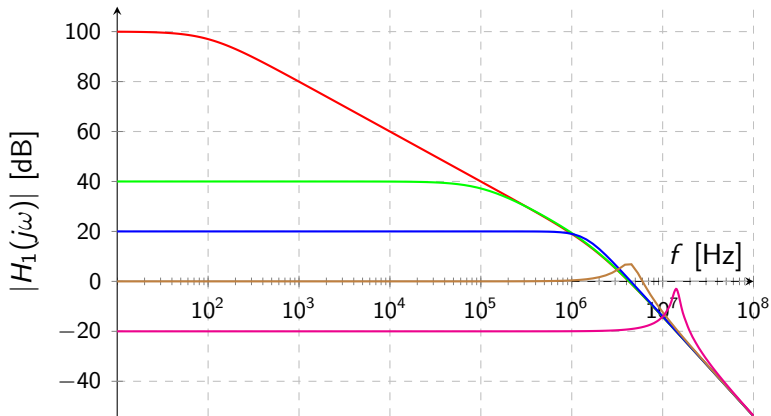
Magnitude frequency responses of the feedback system  $H_1(s)$  for  $\beta = 0, 1/100, 1/10, 1, 10$ .



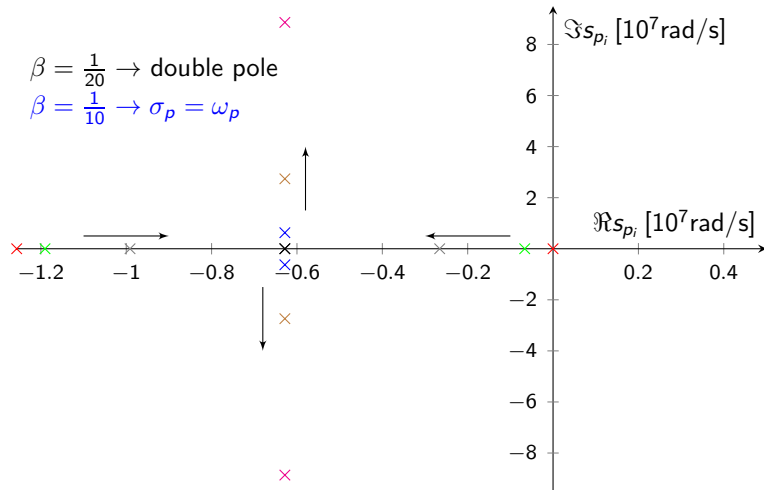
# Active RC (ARC) Filter Synthesis for Cascade Filters

Poles location of the feedback system  $H_1(s)$  for

$\beta = 0, 1/100, 1/30, 1/20, 1/10, 1, 10$ .



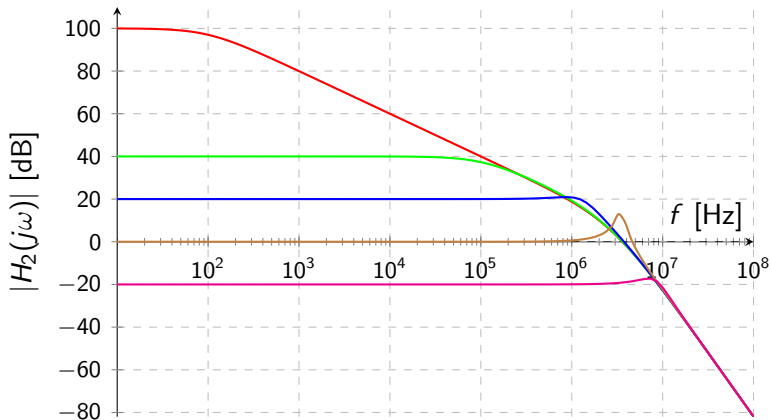Magnitude frequency responses of the feedback system  $H_2(s)$  for  $\beta = 0, 1/100, 1/10, 1, 10$ .




# Active RC (ARC) Filter Synthesis for Cascade Filters

Poles location of the feedback system  $H_2(s)$  for  
 $\beta = 0, 1/100, 1/40, 1/26, 1/15, 3/5, 1$ .

$$\beta \doteq \frac{1}{26} \rightarrow \text{double pole}$$

$$\beta \doteq \frac{1}{15} \rightarrow \sigma_p = \omega_p$$
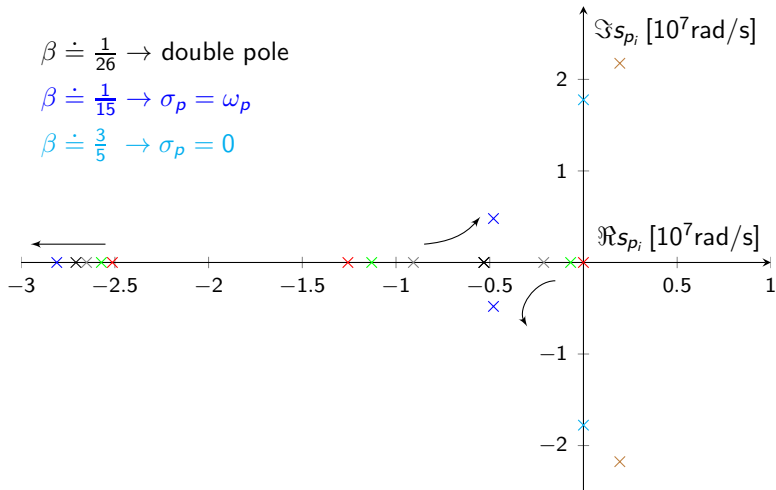
$$\beta \doteq \frac{3}{5} \rightarrow \sigma_p = 0$$




## Biquad Realization using Circuits Working in Continuous Time

- Single amplifier Sallen-Key circuit for LP, HP and BP filters with a small  $Q$ -factor
- Generalized Impedance Converter (GIC) biquad for BP filters with  $Q < 60$ .
- Åckerberg-Mossberg (AM) or Tow-Thomas (TT) circuit for LP and BP filters with higher  $Q$ -factors.
- General biquad based on the TT circuit for elliptic and HP filters.
- Alternatively a single amplifier circuit using double T-network for elliptic filters with small  $Q$ -factors.



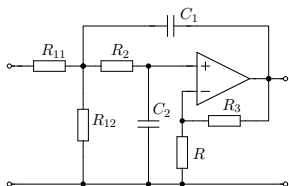
# Active RC (ARC) Filter Synthesis for Cascade Filters


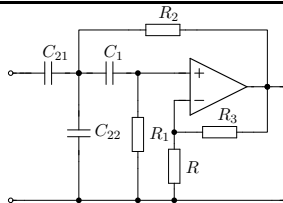
## LP1

metod "K=1":  $C_1, [R, A_0, f_t], (Q < 5)$


metod "min.  $\Gamma_K^Q$ ":  $C_1, C_2, [R, A_0, f_t], (Q < 10)$


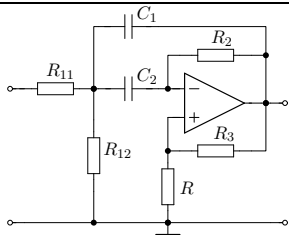
## HP1

metod "K=1":  $C_1, [R, A_0, f_t], (Q < 5)$


metod "min.  $\Gamma_K^Q$ ":  $C_1, C_2, [R, A_0, f_t], (Q < 10)$


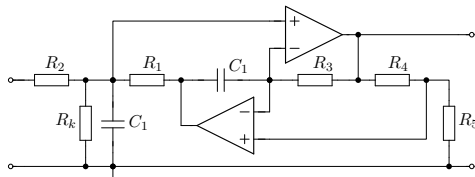
## BP1

metod "K=1":  $C_1, [R, A_0, f_t], (Q < 5)$


metod "min.  $\Gamma_K^Q$ ":  $C_1, C_2, [R, A_0, f_t], (Q < 15)$




## BP2

$C_1, [A_0, f_t], (Q < 60)$
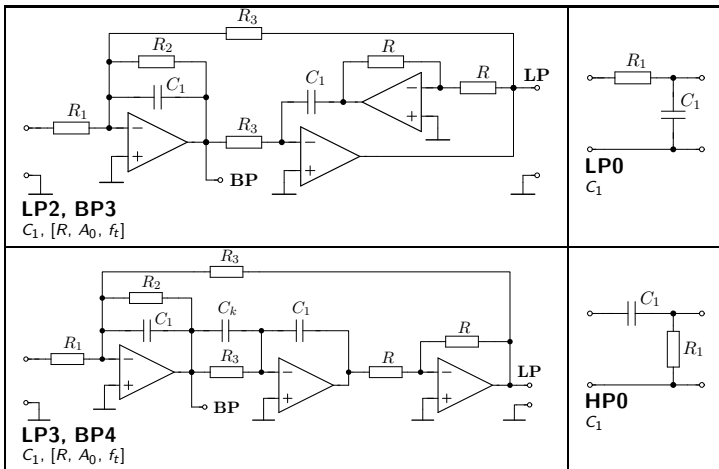
# Active RC (ARC) Filter Synthesis for Cascade Filters




# Active RC (ARC) Filter Synthesis for Cascade Filters

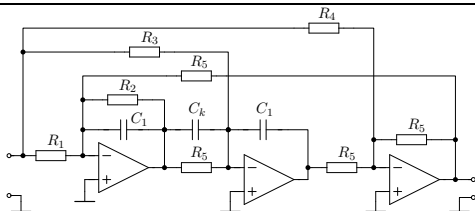


**ES1**

$C_1, [R, A_0, f_t]$

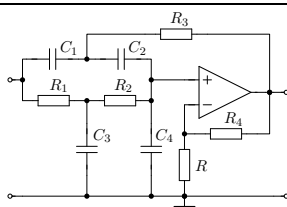


**ESLP**

$C_1, C_2, R, [A_0, f_t]$

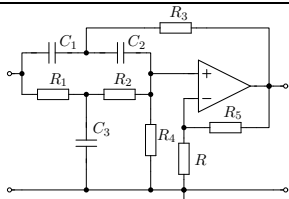

**ESHP**


$C_1, C_2, R, [A_0, f_t]$

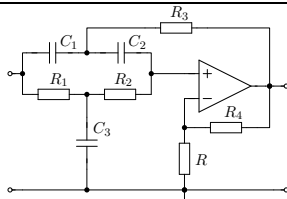

**ESNotch**

$C_1, C_2, R, [A_0, f_t]$

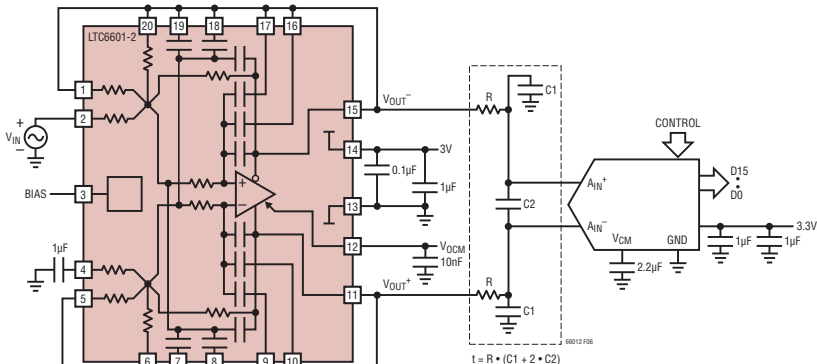
**Example of biquad realization, LTC6601 – pin configurable gain and filter response up to 27MHz: anti-aliasing filter for ADC.**



**ARC filters:** very good dynamic range at low frequencies, tuning is problem.

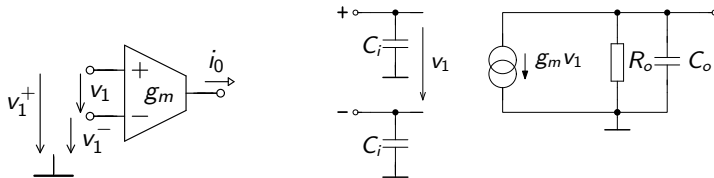
## New blocks for analog filter design

OTA – Operational Transconductance Amplifier




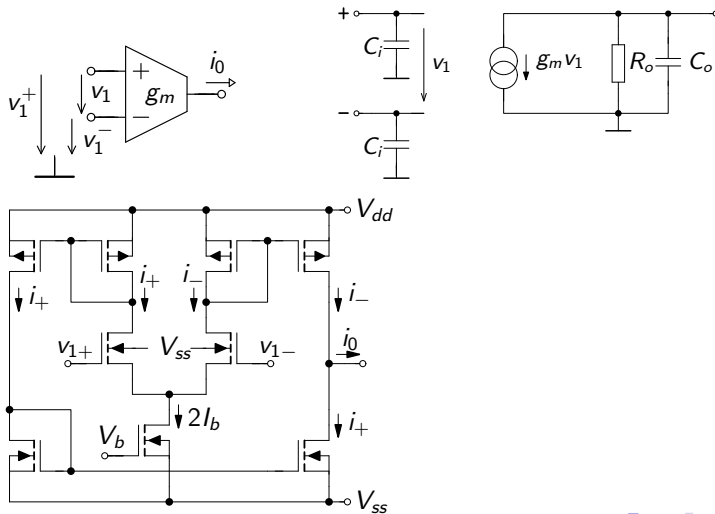
## New blocks for analog filter design

OTA – Operational Transconductance Amplifier


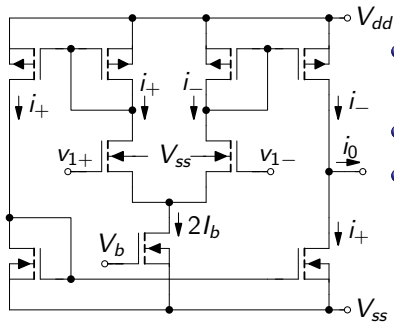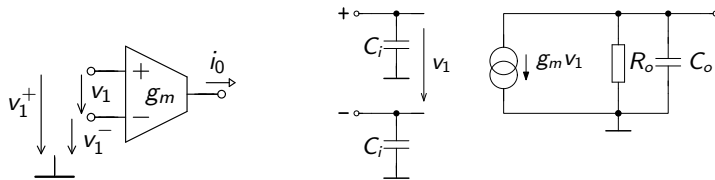
## New blocks for analog filter design

OTA – Operational Transconductance Amplifier




- $C_i = 100^1 \text{ fF}$ ,  $C_o = 100^1 \text{ fF}$  to  $10^0 \text{ pF}$ ,
- $g_m = 10^1 \mu\text{S}$ ,  $g_o = 10^1 \text{ nS}$ ,
- OPA860: B 80 MHz, SR 900 V/ $\mu\text{s}$ ,  $g_m$  95 mS, bipolar OT for wide-bandwidth systems (video and RF, IF circuitry).

## New blocks for analog filter design

OTA – Operational Transconductance Amplifier


OTA integrator

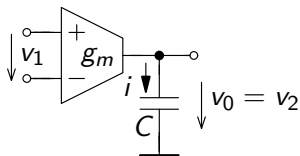

$$\begin{aligned} v_0(t) &= \frac{1}{C} \int i(t) dt = \\ &= \frac{1}{C} \int g_m v_1(t) dt \end{aligned}$$

$$H(s) = \frac{v_2}{v_1} = \frac{g_m}{sC}$$

OTA damped integrator

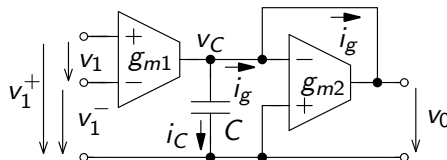


$$i_g = g_{m2} v_C \Rightarrow \frac{v_C}{i_g} = \frac{1}{g_{m2}}$$

$$v_0 = \frac{g_{m1}}{sC + g_{m2}} (v_1^+ - v_1^-)$$



## New blocks for analog filter design

CC – Current Conveyor

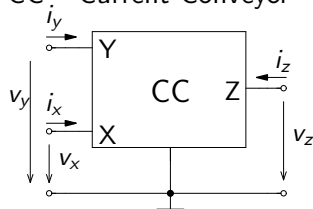


$$v_x = v_y, \quad i_z = \pm i_x, \quad i_y = \alpha i_x,$$

- $\alpha \leq 1$ , CCI,
- $\alpha = 0$ , CCII,
- $\alpha = -1$ , CCIII.


## New blocks for analog filter design

CC – Current Conveyor

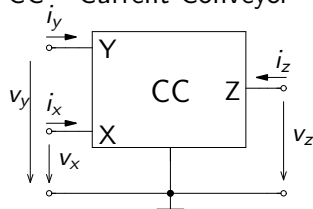


$$v_x = v_y, \quad i_z = \pm i_x, \quad i_y = \alpha i_x,$$

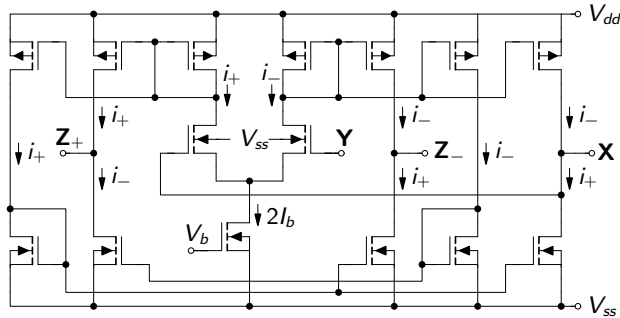- $\alpha \leq 1$ , CCI,
- $\alpha = 0$ , **CCII**,
- $\alpha = -1$ , CCIII.




## New blocks for analog filter design

CC – Current Conveyor

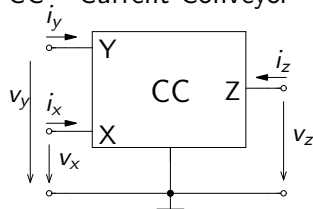


$$v_x = v_y, \quad i_z = \pm i_x, \quad i_y = \alpha i_x,$$

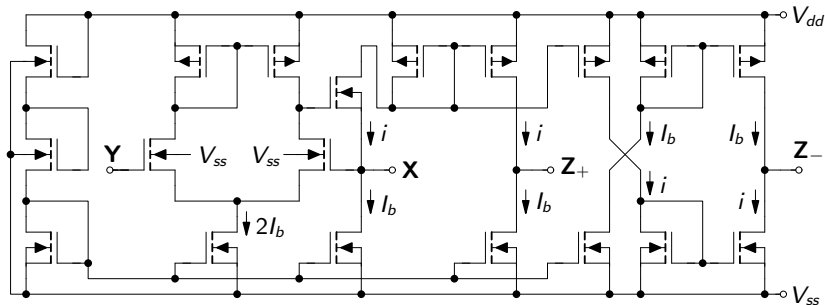- $\alpha \leq 1$ , CCI,
- $\alpha = 0$ , **CCII**,
- $\alpha = -1$ , CCIII.




## New blocks for analog filter design

CC – Current Conveyor

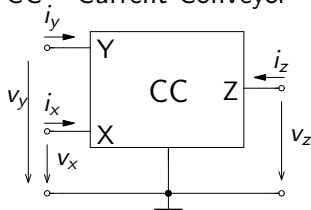


$$v_x = v_y, i_z = \pm i_x, i_y = \alpha i_x,$$

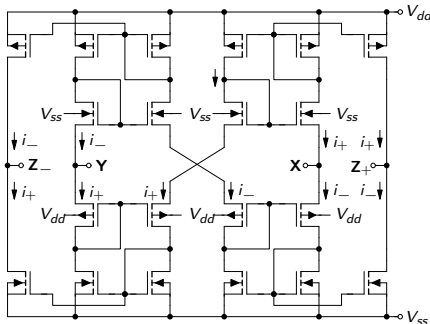- $\alpha \leq 1$ , CCI,
- $\alpha = 0$ , CCII,
- $\alpha = -1$ , **CCIII**.




## New blocks for analog filter design

CC – Current Conveyor

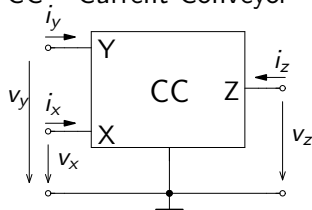

$$v_x = v_y, \quad i_z = \pm i_x, \quad i_y = \alpha i_x,$$


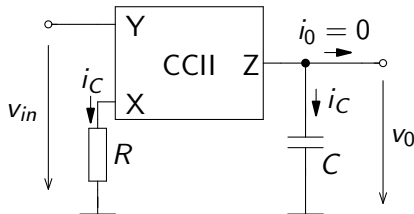
- $\alpha \leq 1$ , CCI,
- $\alpha = 0$ , CCII,
- $\alpha = -1$ , CCIII.




$$v_0(t) = \frac{1}{C} \int i_C(t) dt = \frac{1}{RC} \int v_{in}(t) dt$$

$$H(s) = \frac{V_2}{V_1} = \frac{1}{sCR}$$


## Biquad realization using ARC, OTA

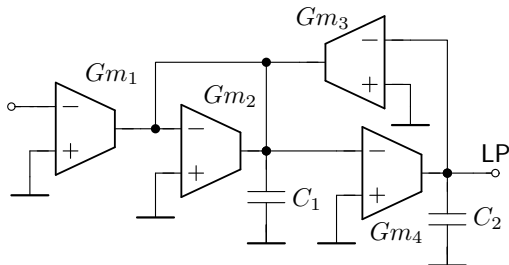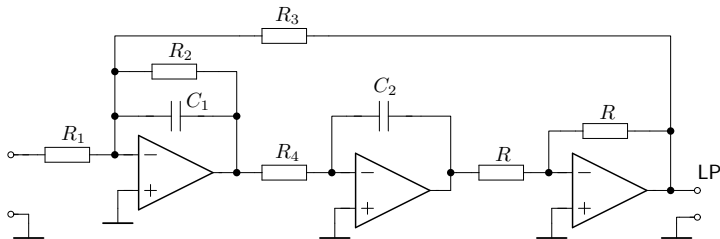
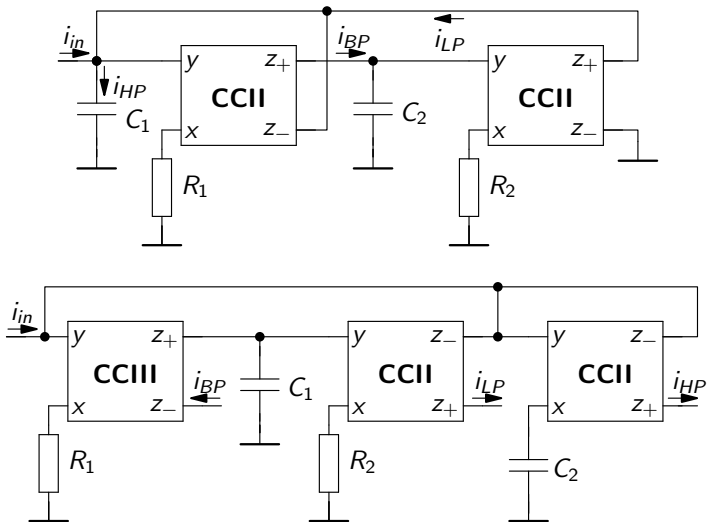
## Biquad realization in "mixed" current mode using CC


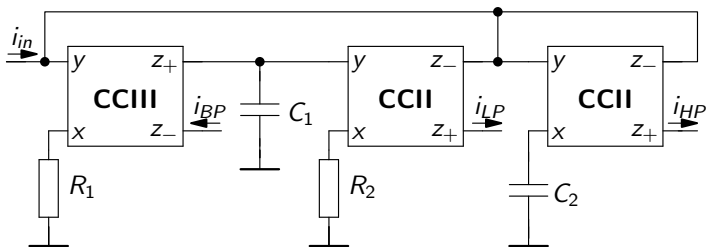
## Biquad realization in "mixed" current mode using CC




$$\frac{i_{LP}}{i_{in}} = \frac{1}{s^2 R_1 R_2 C_1 C_2 + s R_1 C_1 + 1}, \quad \frac{i_{BP}}{i_{in}} = \frac{s R_1 C_1}{s^2 R_1 R_2 C_1 C_2 + s R_1 C_1 + 1}$$

$$\frac{i_{HP}}{i_{in}} = \frac{s^2 R_1 R_2 C_1 C_2}{s^2 R_1 R_2 C_1 C_2 + s R_1 C_1 + 1}, \quad \frac{i_{BS}}{i_{in}} = \frac{i_{LP} + i_{HP}}{i_{in}} =$$

$$= \frac{s^2 R_1 R_2 C_1 C_2 + 1}{s^2 R_1 R_2 C_1 C_2 + s R_1 C_1 + 1}, \quad \frac{i_{AP}}{i_{in}} = \frac{i_{LP} + i_{HP} - i_{BP}}{i_{in}}$$


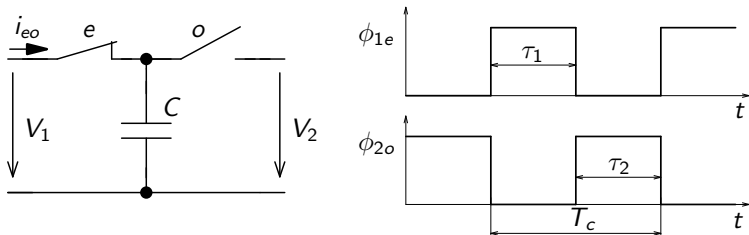
## Principle of Switched Capacitor Circuits




$$Q_1 = C V_1, \quad Q_2 = C V_2, \Rightarrow \Delta Q = Q_1 - Q_2 = C(V_1 - V_2)$$

Relation for equivalent average current  $i_{eo}$  in one switched period  $T_c = 1/f_c$  can be derived


$$i_{eo} = \frac{\partial Q}{\partial t} \doteq \frac{\Delta Q}{\Delta t} = \frac{C(V_1 - V_2)}{T_c} \Rightarrow \frac{V_1 - V_2}{R_{SC}} \Rightarrow R_{SC} = \frac{1}{f_c C}.$$
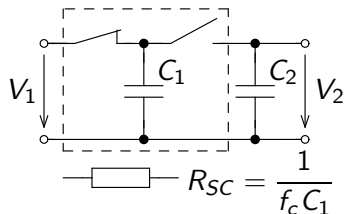
## Principle of Switched Capacitor Circuits



$$K(\omega) = \frac{V_2}{V_1} = \frac{1}{1 + j\omega R_{SC} C_2} = \frac{1}{1 + j\frac{\omega}{f_c} \frac{C_2}{C_1}}$$

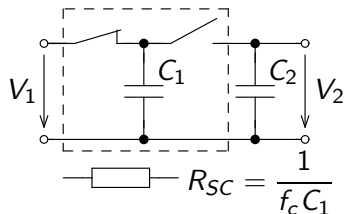
## Principle of Switched Capacitor Circuits



$$K(\omega) = \frac{V_2}{V_1} = \frac{1}{1 + j\omega R_{SC} C_2} = \frac{1}{1 + j\frac{\omega}{f_c} \frac{C_2}{C_1}}$$

$$\omega_0 \sim \frac{f_c C_1}{C_2}$$
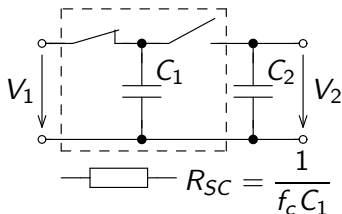
## Principle of Switched Capacitor Circuits




$$K(\omega) = \frac{V_2}{V_1} = \frac{1}{1 + j\omega R_{SC} C_2} = \frac{1}{1 + j\frac{\omega}{f_c} \frac{C_2}{C_1}}$$

$$\omega_0 \sim \frac{f_c C_1}{C_2}$$

- Easy tunable, easy to integrate!
- high accuracy only for ratio's of  $C_i$ , could be 0.2 %,
- possibility to realize high values of resistance ( $f_c = 100$  kHz and  $C = 1$  pF  $\rightarrow 10$  M $\Omega$ ),
- only capacitors to drive  $\rightarrow$  low power,
- only for  $f \ll f_c$ .
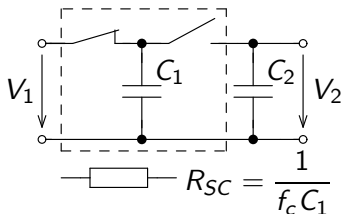
## Principle of Switched Capacitor Circuits




$$K(\omega) = \frac{V_2}{V_1} = \frac{1}{1 + j\omega R_{SC} C_2} = \frac{1}{1 + j\frac{\omega}{f_c} \frac{C_2}{C_1}}$$

$$\omega_0 \sim \frac{f_c C_1}{C_2}$$

- Easy tunable, easy to integrate!
- high accuracy only for ratio's of  $C_i$ , could be 0.2 %,
- possibility to realize high values of resistance ( $f_c = 100$  kHz and  $C = 1$  pF  $\rightarrow 10$  M $\Omega$ ),
- only capacitors to drive  $\rightarrow$  low power,
- only for  $f \ll f_c$ .
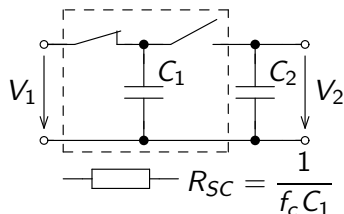
## Principle of Switched Capacitor Circuits




$$K(\omega) = \frac{V_2}{V_1} = \frac{1}{1 + j\omega R_{SC} C_2} = \frac{1}{1 + j\frac{\omega}{f_c} \frac{C_2}{C_1}}$$

$$\omega_0 \sim \frac{f_c C_1}{C_2}$$

- Easy tunable, easy to integrate!
- high accuracy only for ratio's of  $C_i$ , could be 0.2 %,
- possibility to realize high values of resistance ( $f_c = 100$  kHz and  $C = 1$  pF  $\rightarrow 10$  M $\Omega$ ),
- only capacitors to drive  $\rightarrow$  low power,
- only for  $f \ll f_c$ .
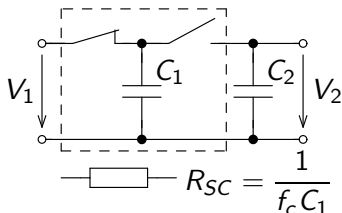
## Principle of Switched Capacitor Circuits




$$K(\omega) = \frac{V_2}{V_1} = \frac{1}{1 + j\omega R_{SC} C_2} = \frac{1}{1 + j\frac{\omega}{f_c} \frac{C_2}{C_1}}$$

$$\omega_0 \sim \frac{f_c C_1}{C_2}$$

- Easy tunable, easy to integrate!
- high accuracy only for ratio's of  $C_i$ , could be 0.2 %,
- possibility to realize high values of resistance ( $f_c = 100$  kHz and  $C = 1$  pF  $\rightarrow 10$  M $\Omega$ ),
- only capacitors to drive  $\rightarrow$  low power,
- only for  $f \ll f_c$ .
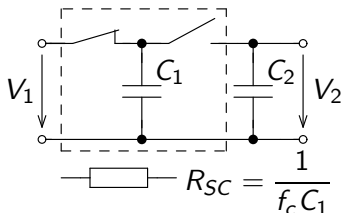
## Principle of Switched Capacitor Circuits





$$K(\omega) = \frac{V_2}{V_1} = \frac{1}{1 + j\omega R_{SC} C_2} = \frac{1}{1 + j\frac{\omega}{f_c} \frac{C_2}{C_1}}$$

$$\omega_0 \sim \frac{f_c C_1}{C_2}$$


- Easy tunable, easy to integrate!
- high accuracy only for ratio's of  $C_i$ , could be 0.2 %,
- possibility to realize high values of resistance ( $f_c = 100$  kHz and  $C = 1$  pF  $\rightarrow 10$  M $\Omega$ ),
- only capacitors to drive  $\rightarrow$  low power,
- only for  $f \ll f_c$ .


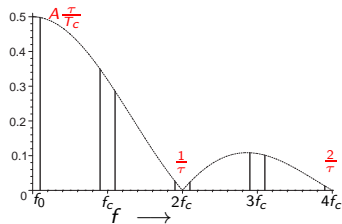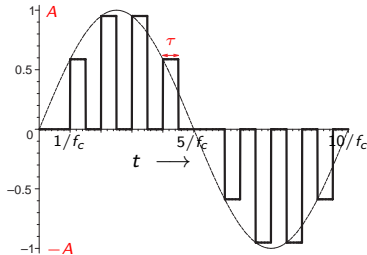
## Spectrum of switched sinusoidal signal


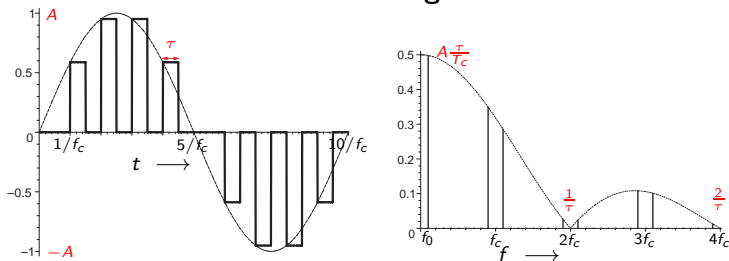
## Spectrum of switched sinusoidal signal




$$\approx A \frac{\tau}{T_c} \sum_{k=0}^{\infty} \frac{\sin(k\omega_c \pm \omega_0) \frac{\tau}{2}}{(k\omega_c \pm \omega_0) \frac{\tau}{2}} \sin((k\omega_c \pm \omega_0)t + \varphi(k))$$

- Spectrum of sampled signal is periodical – period given by  $f_c$ .
- The spectrum is constrictive with factor  $\frac{\tau}{T_c} \frac{\sin(\pi f \tau)}{\pi f \tau}$ ,
- i.e.  $\frac{1}{2} \frac{\sin(\frac{\pi f}{2f_c})}{\frac{\pi f}{2f_c}}$  for  $\tau = T_c/2$ .
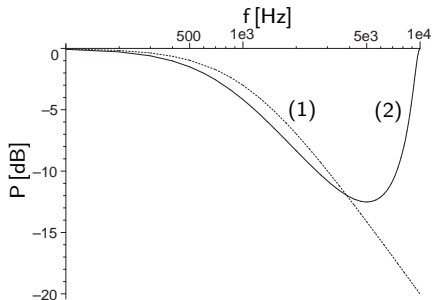
## Frequency response

$$\frac{V_3}{V_1} = \frac{1}{1 + j\omega C_2 R_{eq}} = \frac{1}{1 + j\frac{\omega}{f_c} \frac{C_2}{C_1}} \quad (1)$$

$$K_{13} = \frac{V_{3e}}{V_{1e}} = \frac{C_1}{z(C_1 + C_2) - C_2}, \quad z = e^{j\omega T_c} \quad (2)$$




for  $f_c = 10^4$  [Hz],  $C_1 = 6,2$  [nF] and  $C_2 = 10$  [nF].
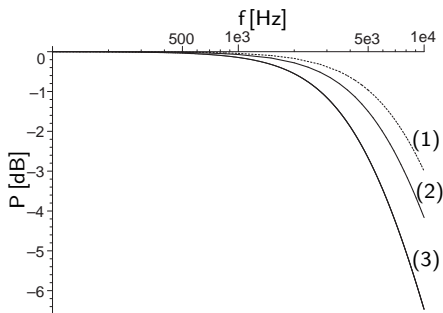
## Frequency response

$$\frac{V_3}{V_1} = \frac{1}{1 + j\omega C_2 R_{eq}} = \frac{1}{1 + j\frac{\omega}{f_c} \frac{C_2}{C_1}} \quad (1)$$



$$K_{13} = \frac{V_{3e}}{V_{1e}} = \frac{C_1}{z(C_1 + C_2) - C_2}, \quad z = e^{j\omega T_c} \quad (2)$$



$$R_{on} = 5 \text{ k}\Omega \quad (3)$$



for  $f_c = 10^5$  [Hz],  $C_1 = 6,2$  [nF] and  $C_2 = 10$  [nF].

## Biquad realization using ARC, SC

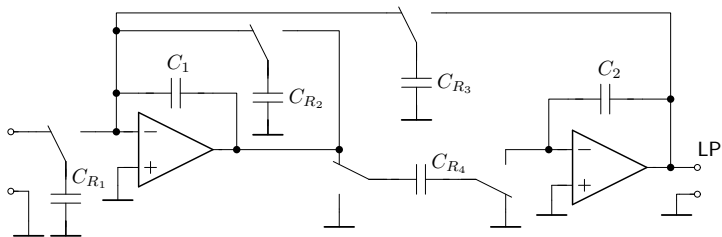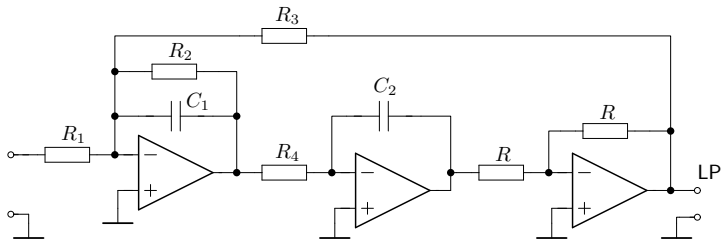

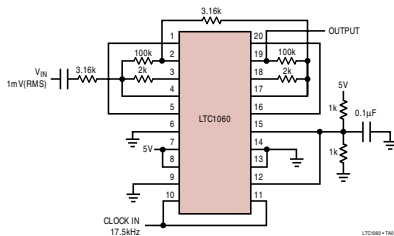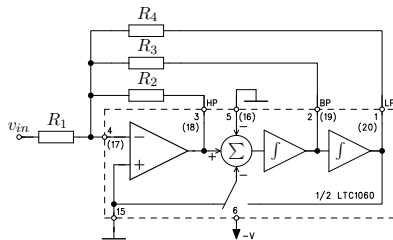
## Realization using Switched Capacitor Circuits based on LTC1060 Chip

- LTC1060 consists of two SC biquads
- LP, HP, BP, BS and allpass
- operates up to 30 kHz ( $f_{clk} = 1.5 \text{ MHz}$ )
- center frequency Q-product up to 1.6 MHz
- 88 dB dynamic range at  $\pm 2.5 \text{ V}$  supply


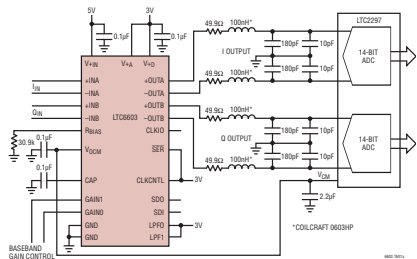
## Example of SC filter realization, LTC6603 – programmable lowpass filter for communications receivers and transmitters




BW up to 2.5MHz


Gain (0/6/12/24 dB)
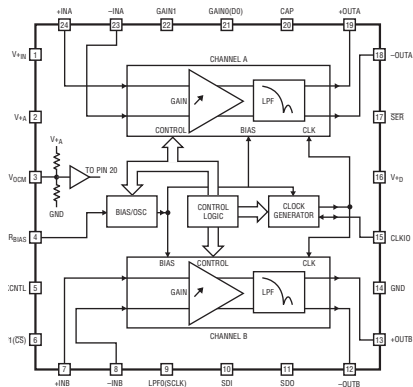
## 9th Order Linear Phase Response

APP.: WCDMA, UMTS, radio links, modems, 802.11x receivers


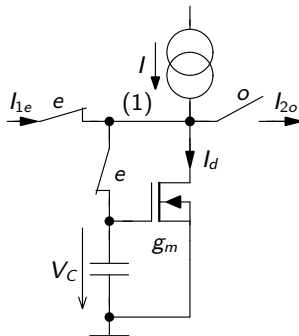
## Principle of Switched Current Circuits





$$\Phi_1 : t = (n - 1/2) T_c \quad I_d = I_{1e}((n - 1/2) T_c) + I$$

$$\Phi_2 : t = (n) T_c \quad I_{2o} = I - I_d = -I_{1e}((n - 1/2) T_c)$$


$$I_{2o}(z) = -z^{-1/2} I_{1e}(z) \quad \Rightarrow \quad \frac{I_{2o}(z)}{I_{1e}(z)} = -z^{-1/2} = -\frac{1}{\sqrt{z}}$$



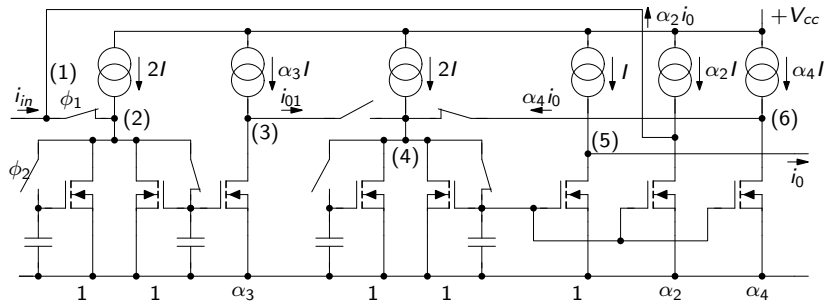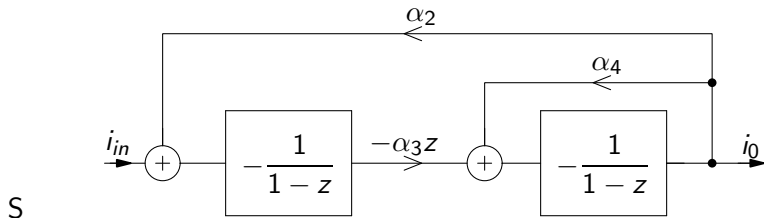
## Biquad realization in "clear" current mode using SI


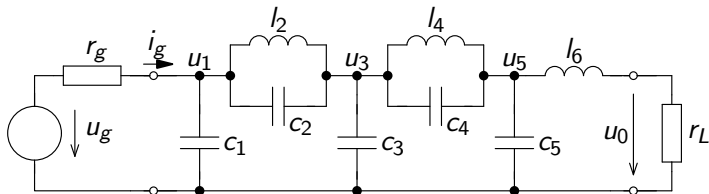
## Active realization of the LC ladder by OTAs


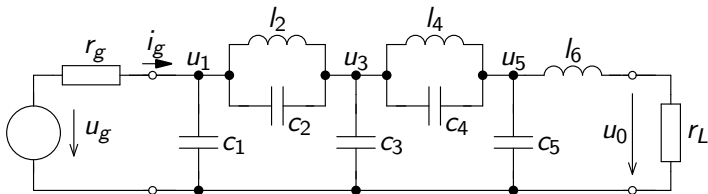
## Active realization of the LC ladder by OTAs



$$v_g = \frac{R}{r_g}(u_g - u_1); \quad u_1 = \frac{1}{sc_1 R}(v_g - v_2 - sc_2 R(u_1 - u_3));$$

$$v_2 = \frac{R}{sl_2}(u_1 - u_3); \quad u_3 = \frac{1}{sc_3 R}(v_2 - v_4 + sc_2 R(u_1 - u_3) - sc_4 R(u_3 - u_5));$$

$$v_4 = \frac{R}{sl_4}(u_3 - u_5); \quad u_5 = \frac{1}{sc_5 R}(v_4 - v_6 + sc_4 R(u_3 - u_5));$$

$$v_6 = \frac{R}{sl_6}(u_5 - u_7); \quad u_7 = \frac{r_2}{R}v_6.$$


## Active realization of the LC ladder by OTAs

$$v_g = \frac{R}{r_g}(u_g - u_1); \quad u_1 = \frac{1}{sc_1 R}(v_g - v_2 - sc_2 R(u_1 - u_3));$$


$$v_2 = \frac{R}{sl_2}(u_1 - u_3); \quad u_3 = \frac{1}{sc_3 R}(v_2 - v_4 + sc_2 R(u_1 - u_3) - sc_4 R(u_3 - u_5));$$

$$v_4 = \frac{R}{sl_4}(u_3 - u_5); \quad u_5 = \frac{1}{sc_5 R}(v_4 - v_6 + sc_4 R(u_3 - u_5));$$
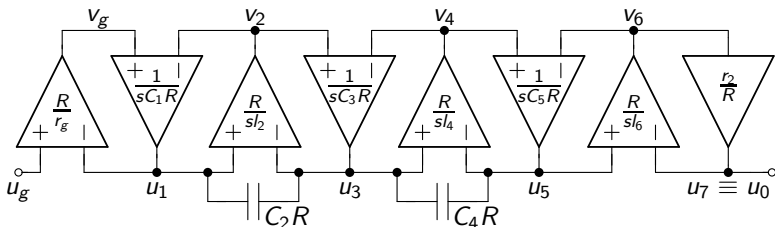
$$v_6 = \frac{R}{sl_6}(u_5 - u_7); \quad u_7 = \frac{r_2}{R}v_6.$$


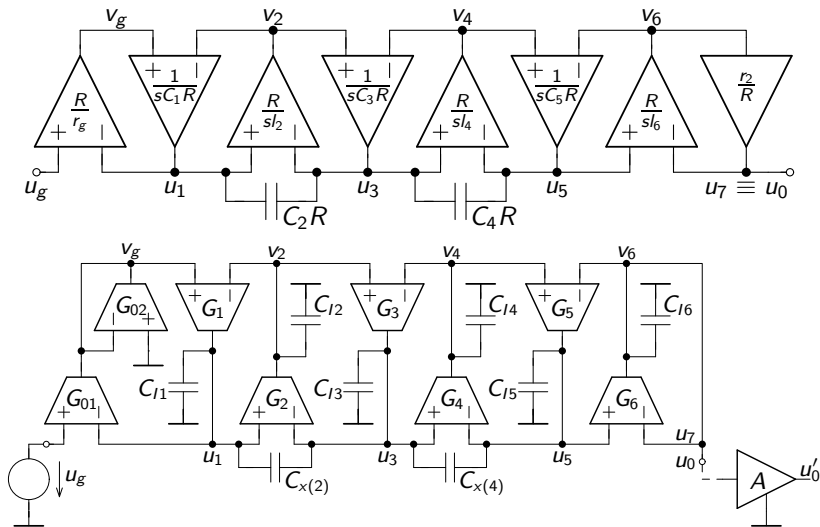
## Active realization of the LC ladder by OTAs



$$C_{lj} = c_j g_{mj} R, j=1,3,5; C_{lk} = l_k g_{mk} / R, k=2,4,6; C_{x(m)} = C_m g_m R, m=2,4.$$



<http://syntfil.feld.cvut.cz>

Filter type choice - Mozilla

File Edit View Go Bookmarks Tools Window Help

Back Forward Reload Stop <http://obvody.feld.cvut.cz/syntfil?cislo=18PHPSE> Search Print

Home Bookmarks mozilla.org Latest Builds

## SYNT<sup>hesis</sup> of electrical FILTERs


[ Project :: **Aproximation** :: LC realization :: ARC realization :: Transfer function :: Help ]

### Filter type choice

Filter type

- ☒ Low pass
- ☐ High pass
- ☐ Band pass
- ☐ Band stop

submit

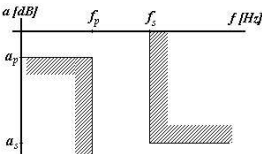

Status

<b>Aproximation</b>	No in progress
<b>LC realization</b>	No in progress
<b>ARC realization</b>	No in progress

(c) FEL ČVUT 2004 [kobon@reznam.cz](mailto:kobon@reznam.cz)

[ [Test & verze](#) | [English version](#) | [Maple](#) ]

## SYNthesis of electrical FILTERs



[ [Project](#) :: [Approximation](#) :: [LC realization](#) :: [ARC realization](#) :: [Transfer function](#) :: [Help](#) ]

## Setting of required values


## Frequency

$f_p =$   Hz

$f_s =$   Hz

$a_p =$   dB

$a_s =$   dB

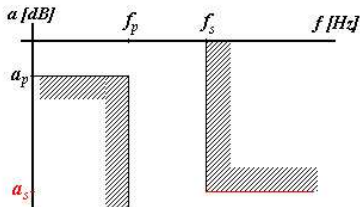

## Status

<b>Approximation</b>	Low pass
<b>LC realization</b>	No in progress
<b>ARC realization</b>	No in progress



## Choosing selection request approximate and order filter

### Approximation

Approximation	Keeping of required parameters			Filter with lower order		
		Order	New value of $a_s$		Order	New value of $a_s$
Butterworth	<input type="radio"/>	8	21.085211	<input type="radio"/>	7	18.195003
Chebyshev	<input checked="" type="radio"/>	4	21.810501	<input type="radio"/>	3	14.449014
Inverzni Chebyshev A	<input type="radio"/>	4	21.810501	<input type="radio"/>	3	14.449014
Inverzni Chebyshev B	<input type="radio"/>	4	21.810501 ( $\Omega_s=1.457638$ )	<input type="radio"/>	2	7.772117 ( $\Omega_s=1.708801$ )
Cauer A	<input type="radio"/>	3	26.194390	<input type="radio"/>	2	12.957894
Cauer B	<input type="radio"/>	4	39.698595 ( $\Omega_s=1.480785$ )	<input type="radio"/>	2	12.957894 ( $\Omega_s=1.825298$ )
Cauer C	<input type="radio"/>	4	39.698595 ( $\Omega_s=1.566231$ )	<input type="radio"/>	2	12.957894 ( $\Omega_s=2.379796$ )

## Result from aproximate analyzis

NLP (Norm Low pass)

### Transfer function

$$H(p) = \frac{0.163445}{1.000000p^4 + 0.716215p^3 + 1.256482p^2 + 0.516798p + 0.205765}$$

graph


### Zeros and poles

Zeros	Poles
	-.104887252238877+.957952960166620*i
	-.104887252238877-.957952960166620*i
	-.253220226875144+.396797108216470*i
	-.253220226875144-.396797108216470*i

graph

### Coefficient Gc

Scheme of LC filter

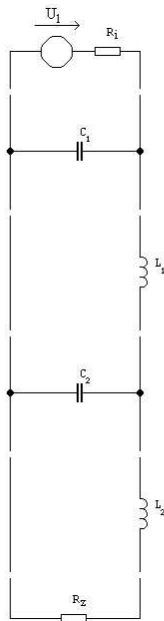

$$R_i = 1k \text{ } [\Omega]$$

$$C_1 = 88.887n \text{ } [F]$$

$$L_1 = 28.03m \text{ } [H]$$

$$Q_1 = \text{infinity} \text{ } [-]$$

$$R_1 = 0 \text{ } [\Omega]$$

$$C_2 = 114.793r \text{ } [F]$$

$$L_2 = 21.704m \text{ } [H]$$

$$Q_2 = \text{infinity} \text{ } [-]$$

$$R_2 = 0 \text{ } [\Omega]$$


$$R_z = 244.177 \text{ } [\Omega]$$

# WWW Interface – ARC Cascade Filter Synthesis

Block - Mozilla

Block 1

Synthesis of ARC block

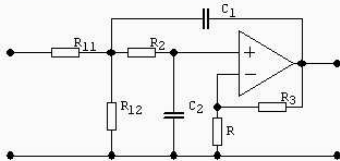

$\omega_0 = 30.275k$   
 $Q = 4.594$   
 $\omega_n = \dots$   
 $h_0 = 216.388m$

$R_{12} = .39e-4$   
type = LP1  
 $C_1 = 10$   
 $A_0 = \text{infinity}$   
 $R_{11} = .15e-3$   
 $f_t = 10000$   
 $R_2 = .30e-4$   
 $R = \text{infinity}$   
 $C_2 = .118462682849835$   
 $R_3 = 0$


Select resistors from series:

$C_1 =$    
 $C_2 =$    
 $R =$    
 $k =$    
 $f_t =$    
 $A_0 =$    
Type =  ?

design

save no save

## Graph

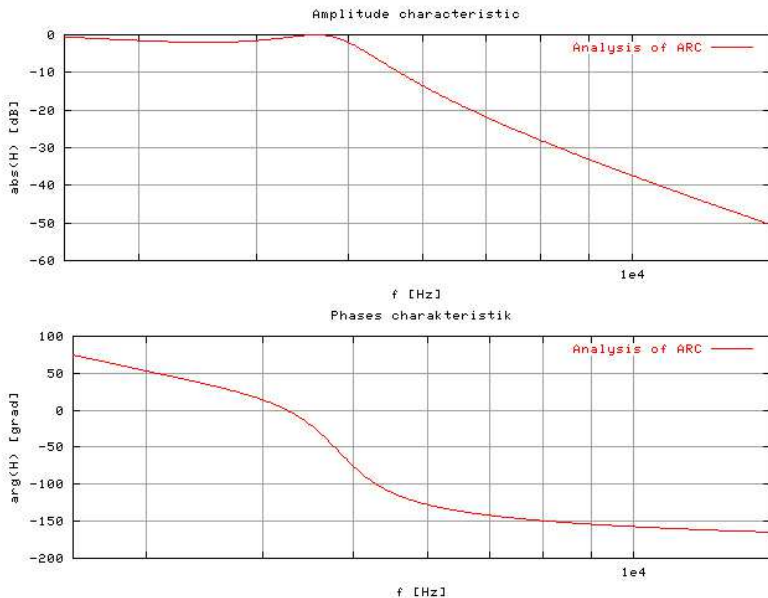

-  Schaumann, R., Valkenburg, M.E.V.: *Design of Analog Filters*. Oxford University Press, 2001.
-  Bičák J., Laipert M., Vlček M.: *Lineární obvody a systémy*, Monografie ČVUT, Praha 2006.
-  Sedra, A. S., Smith, K. C.: *Microelectronic Circuits*, 5th edition, Oxford University Press, Inc., New York 2004. ISBN 0-19-514-251-9.

Thank you for your attention !



KATEDRA TEORIE OBVODŮ  
Fakulta elektrotechnická